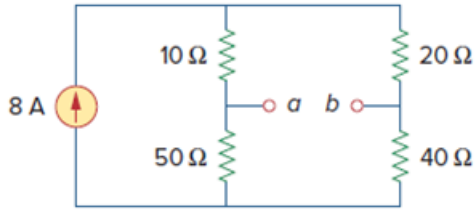


Problem

Determine the Thevenin and Norton equivalents at terminals a - b of the circuit in Fig. 4.125.


Figure. 4.125:



Step-by-step solution

Step 1 of 13


Given circuit diagram

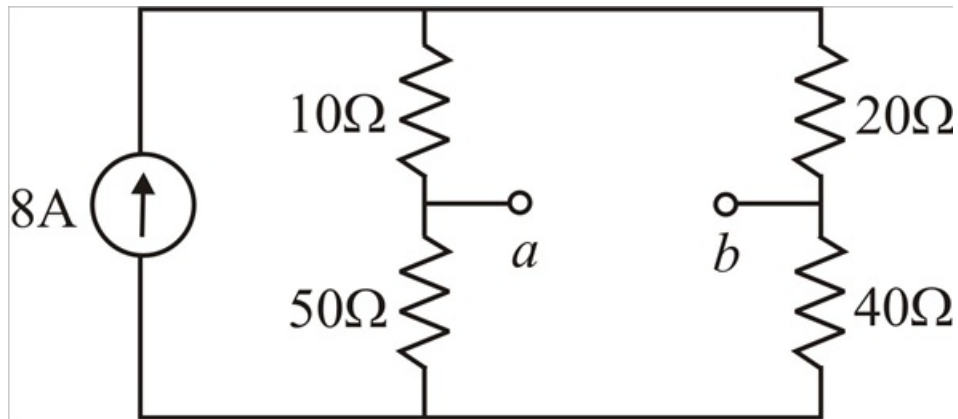

Step 2 of 13

Thevenin's Equivalent Circuit:

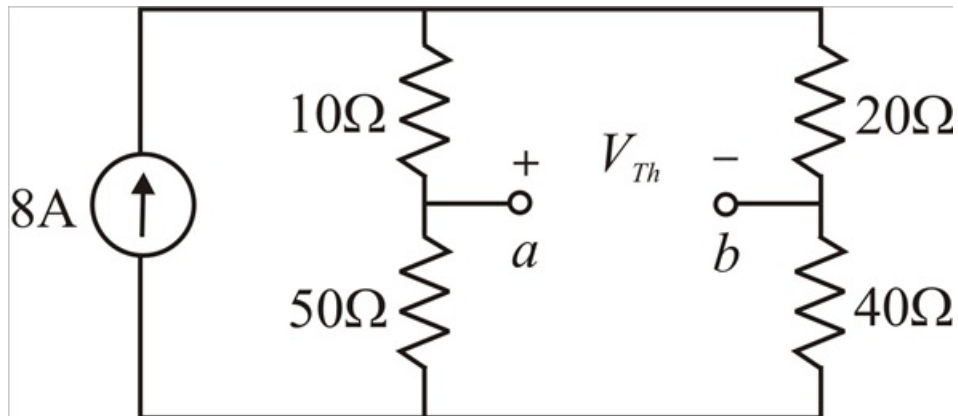To determine Thevenin's equivalent voltage (V_{Th}) between a and b terminals consider below circuit



Step 3 of 13

From the above circuit we can write

$$V_{Th} = V_a - V_b$$

By using current division rule current flowing through 50Ω resistor is

$$I_{50\Omega} = 8 \left(\frac{20 + 40}{20 + 40 + 10 + 50} \right)$$

$$I_{50\Omega} = 8 \left(\frac{60}{120} \right)$$

$$I_{50\Omega} = 4\text{A}$$

From the above circuit

$$V_a = I_{50\Omega} (50)$$

$$V_a = (4)(50)$$

$$V_a = 200\text{V}$$

Step 4 of 13

Current flowing through 40Ω resistor is

$$I_{40\Omega} = 8 - I_{50\Omega}$$

$$I_{40\Omega} = 8 - 4$$

$$I_{40\Omega} = 4\text{A}$$

From the above circuit

$$V_b = I_{40\Omega} (40)$$

$$V_b = (4)(40)$$


$$V_b = 160\text{V}$$

$$V_{Th} = 200 - 160$$

$$\boxed{V_{Th} = 40\text{V}}$$

Step 5 of 13

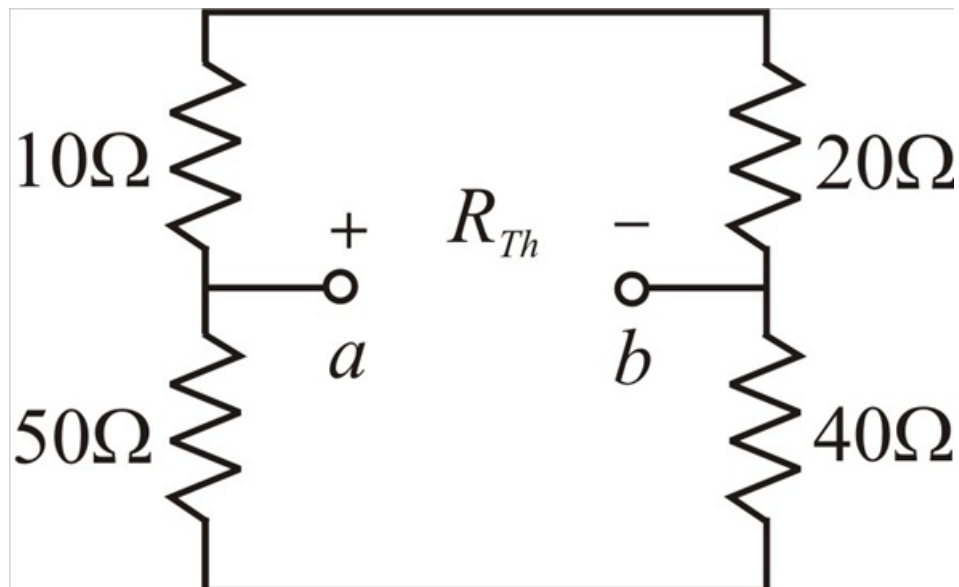To determine Thevenin's resistance (R_{Th}) between a and b terminals consider below circuit



Step 6 of 13

$$R_{Th} = (10 + 20) \parallel (50 + 40)$$


$$R_{Th} = 30 \parallel 90$$

$$R_{Th} = \frac{30 \times 90}{30 + 90}$$

$$R_{Th} = 22.5\Omega$$

Step 7 of 13

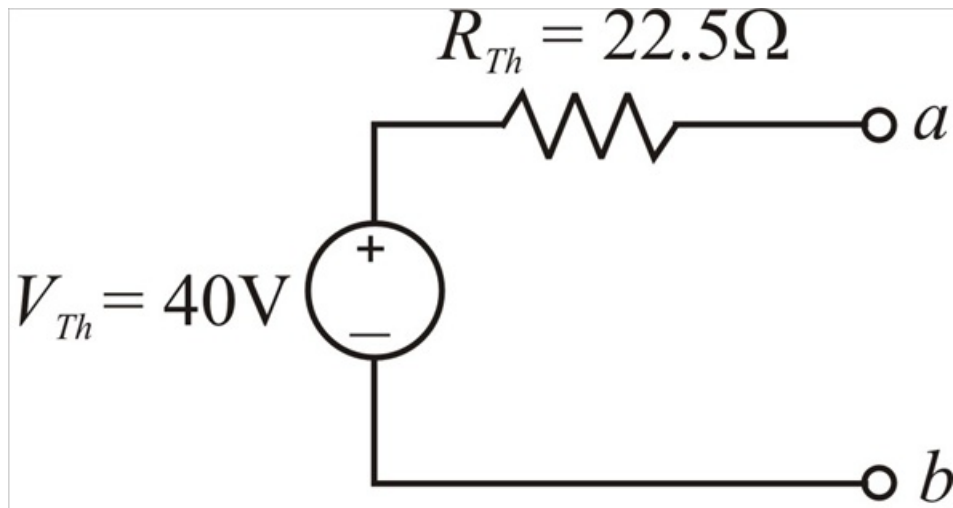
Therefore Thevenin's equivalent circuit between a and b terminals



Step 8 of 13

Norton's Equivalent Circuit:

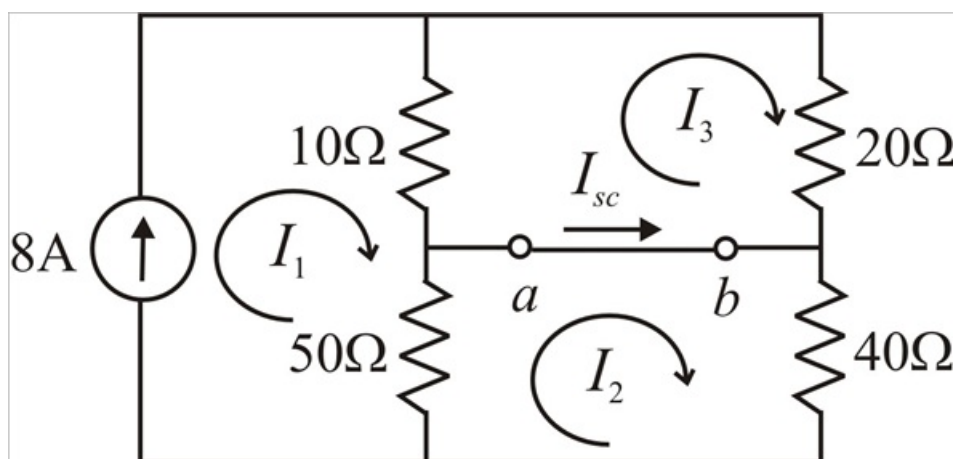To determine Norton's equivalent current (I_N) between a and b terminals consider below circuit



Here $I_N = I_{sc}$ (short circuit current)

Step 9 of 13

From the above circuit

$$I_1 = 8\text{A}$$

$$I_{sc} = I_N = I_2 - I_3$$

Applying KVL to loop 2 gives

$$50(I_2 - I_1) + 40(I_2) = 0$$

$$-50I_1 + 90I_2 = 0$$

$$-50(8) + 90I_2 = 0$$

$$90I_2 = 400$$

$$I_2 = 4.4444\text{A}$$

Step 10 of 13

Applying KVL to loop 3 gives

$$10(I_3 - I_1) + 20(I_3) = 0$$

$$-10I_1 + 30I_3 = 0$$

$$-10(8) + 30I_3 = 0$$

$$30I_3 = 80$$

$$I_3 = 2.6667\text{A}$$


$$I_N = 4.4444 - 2.6667$$

$$I_N = 1.7777\text{A}$$

$$I_N = 1.78\text{A}$$

Step 11 of 13

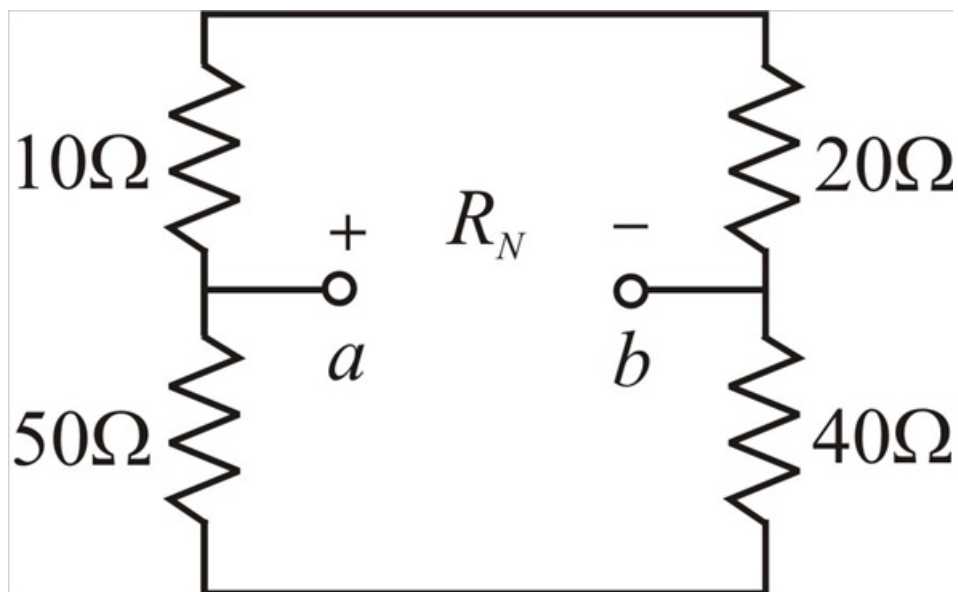To determine Norton's resistance (R_N) between a and b terminals consider below circuit



Step 12 of 13

$$R_N = (10 + 20) \parallel (50 + 40)$$

$$R_N = 30 \parallel 90$$

$$R_N = \frac{30 \times 90}{30 + 90}$$

$$R_N = 22.5\Omega$$

Step 13 of 13

Therefore Norton's equivalent circuit between a and b terminals

