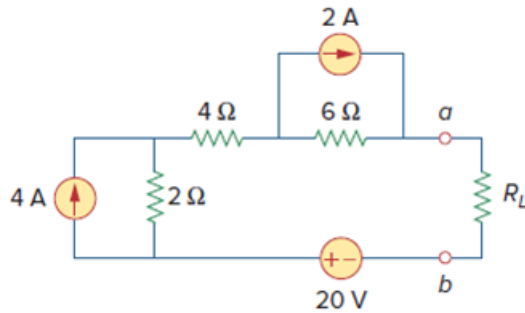


Problem

- (a) For the circuit in Fig. 4.138, obtain the Thevenin equivalent at terminals a - b .
- (b) Calculate the current in $R_L = 13\ \Omega$.
- (c) Find R_L for maximum power deliverable to R_L .
- (d) Determine that maximum power.

Figure 4.138:




Step-by-step solution

Step 1 of 9

Refer to Figure 4.138 in the text book.

(a)

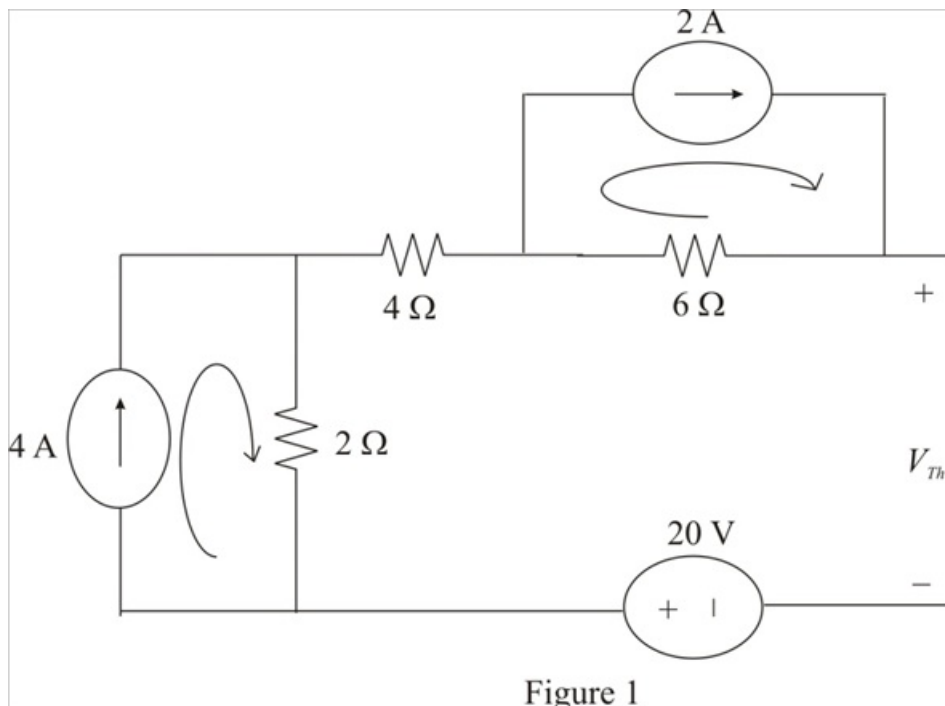Disconnect the load resistance to calculate the Thevenin's voltage.



[Comments \(1\)](#)



Anonymous

Why there is no current in 4ohms? and how come 20V is positive?

Step 2 of 9

Notice that no current flows through $4\ \Omega$ resistor.

Calculate the value of the Thevenin's voltage V_{Th} .

$$\begin{aligned} V_{Th} &= (2)(6) + (4)(2) + 20 \\ &= 12 + 8 + 20 \\ &= 40\text{ V} \end{aligned}$$

Therefore, the value of the Thevenin's voltage V_{Th} is 40 V .

Step 3 of 9

Set the values of the sources to calculate the value of the Thevenin's resistance.

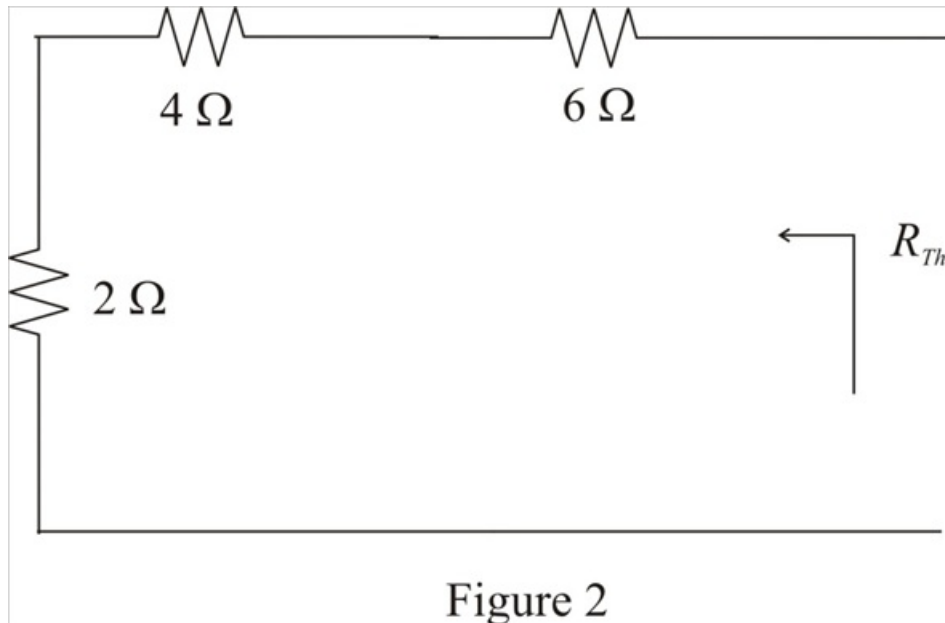


Figure 2

Step 4 of 9

Calculate the value of the Thevenin's resistance R_{Th} .

$$\begin{aligned} R_{Th} &= 6 + 4 + 2 \\ &= 12\ \Omega \end{aligned}$$

Therefore, the value of the Thevenin's resistance R_{Th} is $12\ \Omega$.

Step 5 of 9

Draw the Thevenin's equivalent circuit diagram.

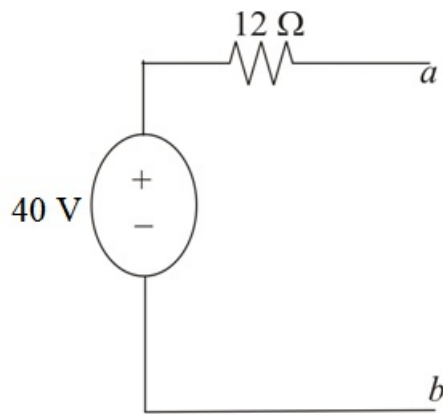


Figure 3

Step 6 of 9

(b)

Connect the load resistance to the Thevenin's circuit as show in Figure 4.

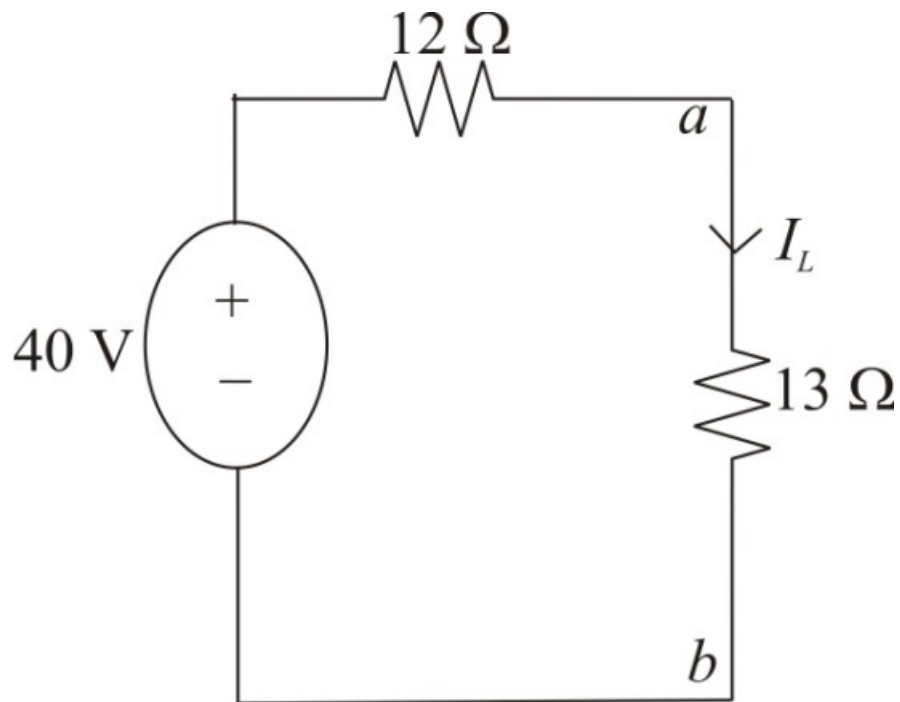


Figure 4

Step 7 of 9

Calculate the value of the load current I_L .

$$\begin{aligned} I_L &= \frac{40}{12+13} \\ &= \frac{40}{25} \\ &= 1.6 \text{ A} \end{aligned}$$

Therefore, the value of the load resistance I_L is 1.6 A.

Step 8 of 9

(c)

For the maximum power to be delivered to the load, the value of the load must be equal to the Thevenin's resistance R_{Th} . Therefore, the value of the load R_L is $12\ \Omega$.

Step 9 of 9

(d)

Calculate the maximum power absorbed by the load.

$$P_{\max} = \frac{V_{Th}^2}{4R_L}$$

Substitute 40 V for V_{Th} and $12\ \Omega$ for R_L .

$$\begin{aligned} P_{\max} &= \frac{(40)^2}{4(12)} \\ &= \frac{1600}{48} \\ &= 33.33\text{ W} \end{aligned}$$

Therefore, the value of the maximum power absorbed by the load is 33.33 W .