

Chapter 4, Problem 76P

Problem

Solve Prob. 4.34 using *PSpice* or *MultiSim*. Let $V = 40\text{ V}$, $I = 3\text{ A}$, $R_1 = 10\ \Omega$, $R_2 = 40\ \Omega$, and $R_3 = 20\ \Omega$.

Step-by-step solution

Step 1 of 3


From the plot, we obtain,

$$V = 92\text{ V [} i = 0, \text{ Voltage axis intercept]}$$

$$R = \text{slope} = \frac{(120 - 92)}{1}$$

$$R = 28\ \Omega$$

Step 2 of 3

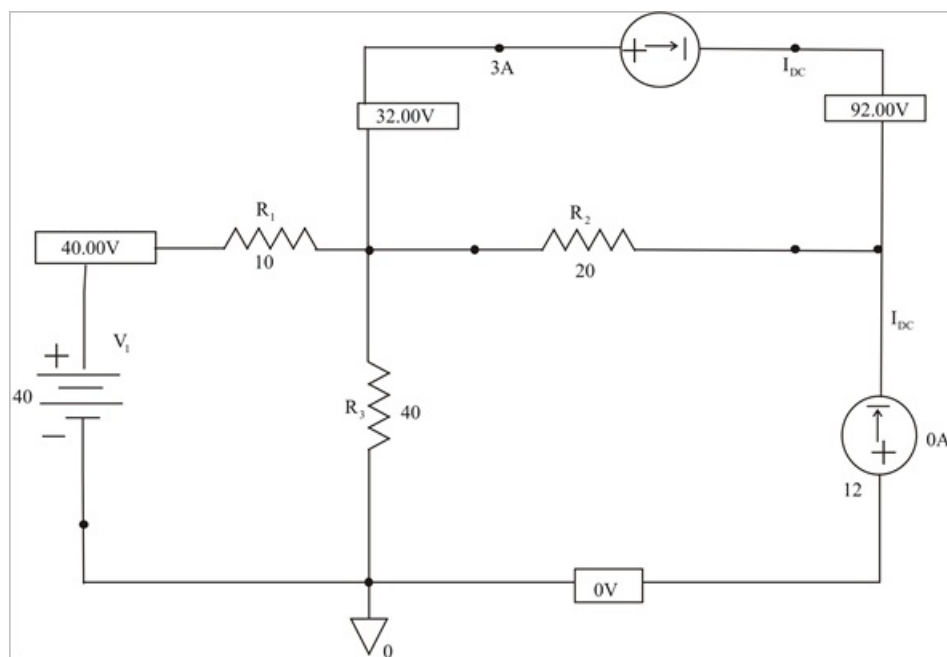

Step 3 of 3

