

Chapter 4, Problem 77P

Problem

Use *PSpice* or *MultiSim* to solve Prob. 4.44.

Step-by-step solution

Step 1 of 3


(A) The schematic is shown below. We perform a DC sweep on a current source, I1 connected between terminals a and b. We label the top and bottom source I1 as 2 and 1 respectively.

We plot $V(2) - V(1)$ as shown.

$$V_{TH} = 4V \text{ [Zero Intercept]} .$$

$$R_{TH} = \frac{(7.8-4)}{1} = 3.8\text{ Ohms} .$$

Step 2 of 3

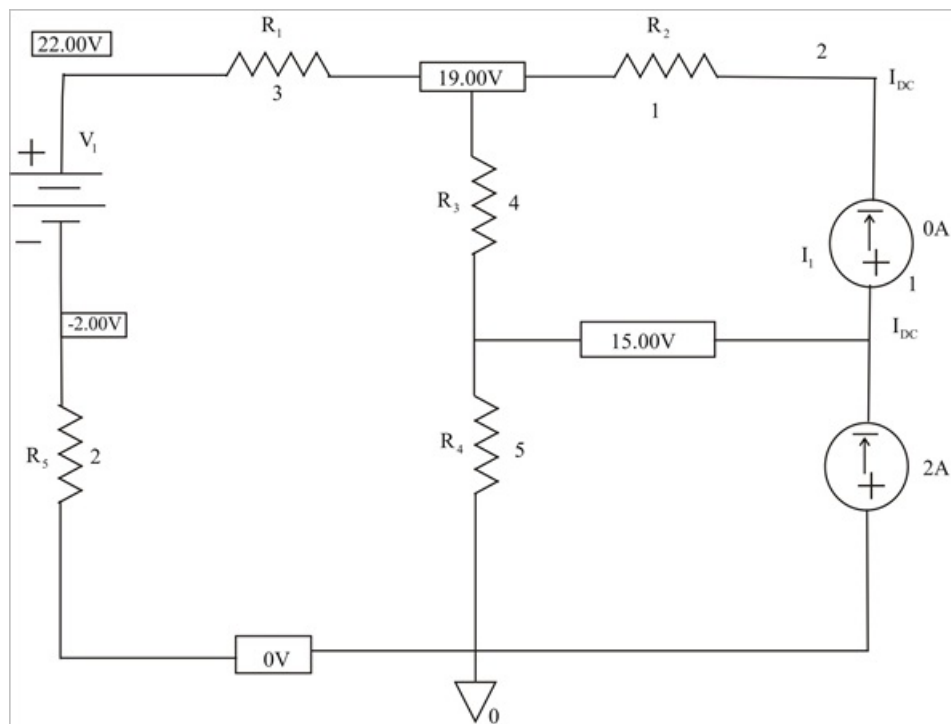

Step 3 of 3

