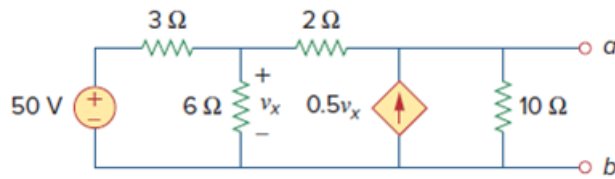


Problem

Obtain the Thevenin equivalent of the circuit in Fig. 4.123 using *PSpice* or *MultiSim*.

Figure. 4.123:



Step-by-step solution

Step 1 of 3


After drawing and saving the schematic as shown below, we perform a DC sweep on I1 connected across a and b. The plot is shown.

From the plot we get,

$$V = 167V \text{ [Zero Intercept] .}$$

$$R = \frac{(177-167)}{1} = 10\text{Ohms} .$$

Step 2 of 3

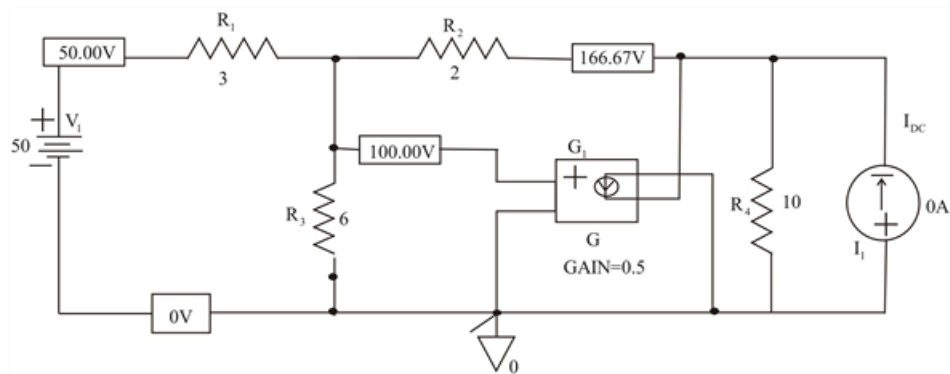

Step 3 of 3

