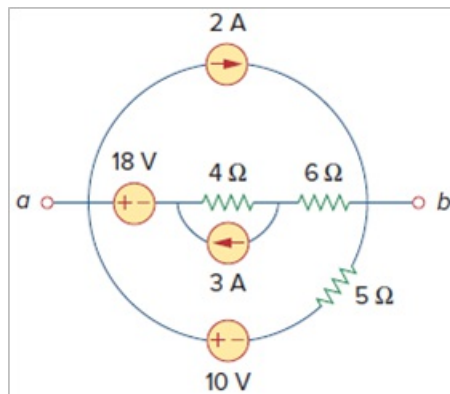


Problem

For the circuit in Fig. 4.126, use *PSpice* or *MultiSim* to find the Thevenin equivalent at terminals *a-b*.

Figure. 4.126:



Step-by-step solution

Step 1 of 2

The schematic is shown below. We perform a DC sweep on the current source, *I2* connected between terminals *a* and *b*. The plot of the voltage across *I2* is shown below.

From the plot,

$$V_{TH} = 10V \text{ [Zero Intercept] .}$$

$$R_{TH} = \frac{(10 - 6.4)}{1} = 3.4 \text{ Ohms .}$$

Step 2 of 2

