

Chapter 4, Problem 82P

Problem

An automobile battery has an open circuit voltage of 14.7 V which drops to 12 V when connected to two 65-W headlights. What is the resistance of the headlights and the value of the internal resistance of the battery?

Step-by-step solution

Step 1 of 4

The value of the Thevenin's voltage is equal to the open circuit voltage. That is,

$$V_{\text{Th}} = 14.7 \text{ V}.$$

Calculate the value of the current passing through 65 W load.

$$\begin{aligned} I &= \frac{65}{12} \\ &= 5.4167 \text{ A} \end{aligned}$$

Therefore, the value of the current I is 5.4167 A.

Step 2 of 4

Calculate the value of the load resistance R_L .

$$R_L = \frac{V}{I}$$


Substitute 5.4167 A for I and 12 V for V .

$$\begin{aligned} R_L &= \frac{12}{5.4167} \\ &= 2.215 \Omega \end{aligned}$$

Therefore, the value of the load resistance R_L is 2.215 Ω .

Step 3 of 4

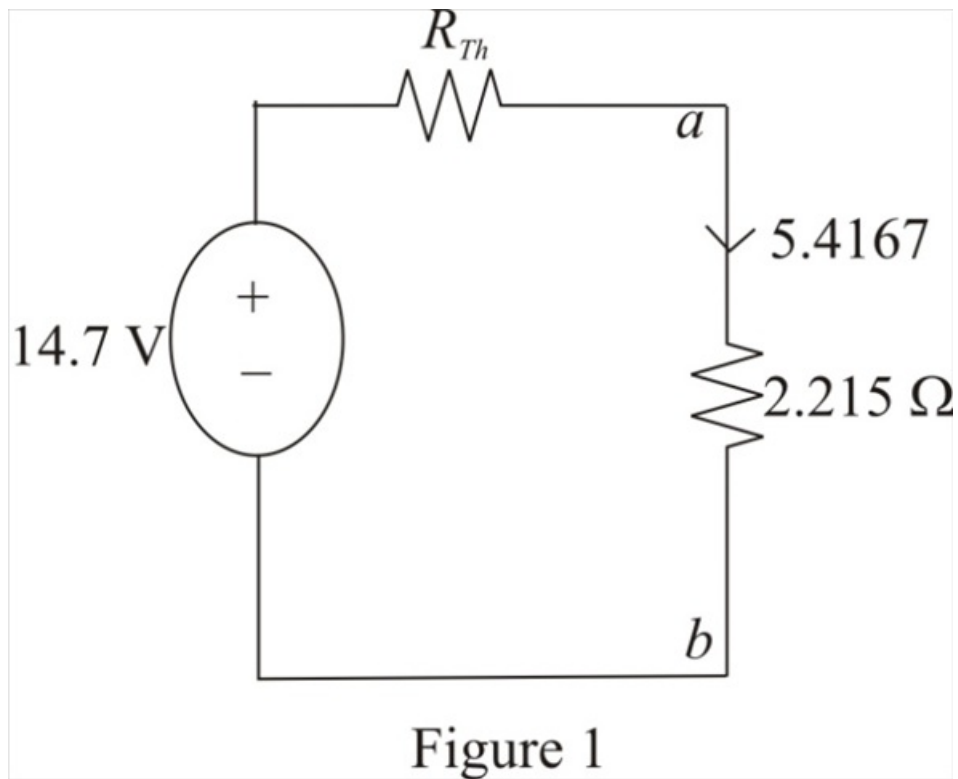Draw the Thevenin's equivalent circuit diagram including the load.



Step 4 of 4

Apply Kirchhoff's voltage law in the circuit.

$$-14.7 + (5.4167)(R_{Th} + 2.215) = 0$$

$$(5.4167)(R_{Th} + 2.215) = 14.7$$

$$R_{Th} + 2.215 = \frac{14.7}{5.4167}$$

$$R_{Th} + 2.215 = 2.7138$$

$$R_{Th} = 2.7138 - 2.215$$

$$= 0.4988$$

$$\approx 0.5 \Omega$$

This value of the Thevenin's resistance is the internal resistance of the circuit.

Therefore, the value of the internal resistance is 0.5Ω .