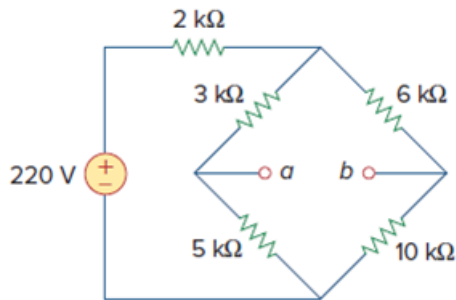


Problem

Consider the bridge circuit of Fig. 4.148. Is the bridge balanced? If the 10-k Ω resistor is replaced by an 18-k Ω resistor, what resistor connected between terminals a - b absorbs the maximum power? What is this power?



Step-by-step solution

Step 1 of 12

Refer to Figure 4.148 in the textbook.

Consider the ratio for a balanced bridge.

$$\frac{P}{Q} = \frac{R}{S} \dots\dots (1)$$

Here,

P , Q , R , and S , are the bridge resistances.

Substitute 3 k Ω for P , 6 k Ω for Q , 5 k Ω for R , and 10 k Ω for S .

$$\frac{3}{6} = \frac{5}{10}$$

$$\frac{1}{2} = \frac{1}{2}$$

Hence, the bridge is **balanced**.

Step 2 of 12

Replace 10 k Ω resistor by 18 k Ω .

Substitute 18 k Ω for S in equation (1).

$$\frac{P}{Q} = \frac{R}{S}$$

$$\frac{3}{6} \neq \frac{5}{18}$$

$$\frac{1}{2} \neq \frac{5}{18}$$

Hence, the bridge is **not balanced** on replacing the resistor of 10 k Ω by 18 k Ω .

Step 3 of 12

Consider the following circuit diagram as shown in Figure 1.

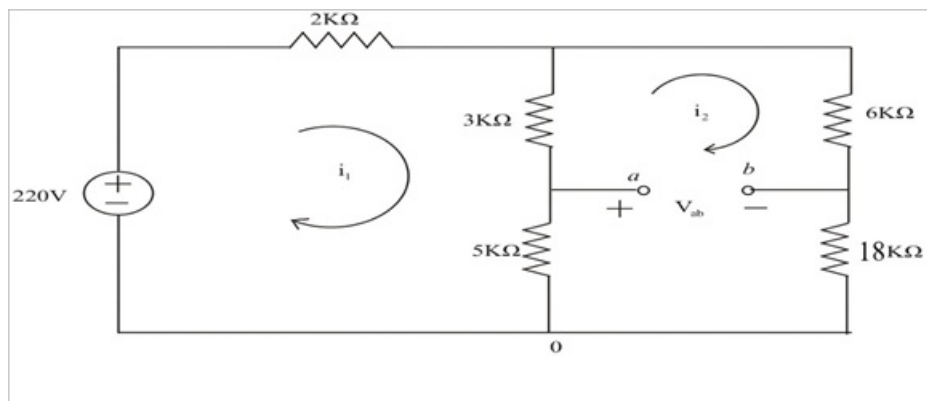


Figure 1

Step 4 of 12

In figure 1.

Here,

i_1 , and i_2 are assumed to be in mA.

Apply KVL in loop 1.

$$220 = 2i_1 + 8(i_1 - i_2)$$

$$220 = 10i_1 - 8i_2 \dots\dots (2)$$

Apply KVL in loop 2.

$$(5+3)(i_2 - i_1) + (6+18)(i_2) = 0$$

$$8(i_2 - i_1) + 24(i_2) = 0$$

$$32i_2 - 8i_1 = 0$$

$$i_1 = 4i_2 \dots\dots (3)$$

Step 5 of 12

Substitute $4i_2$ for i_1 in equation (2).

$$220 = 10i_1 - 8i_2$$

$$220 = 10(4i_2) - 8i_2$$

$$220 = 32i_2$$

$$i_2 = 6.87 \text{ mA}$$

Substitute 6.87 mA for i_2 in equation (3).

$$i_1 = 4i_2$$

$$= 4(6.87)$$

$$= 27.48 \text{ mA}$$

Step 6 of 12

Consider the following circuit, when shorting a, and b.

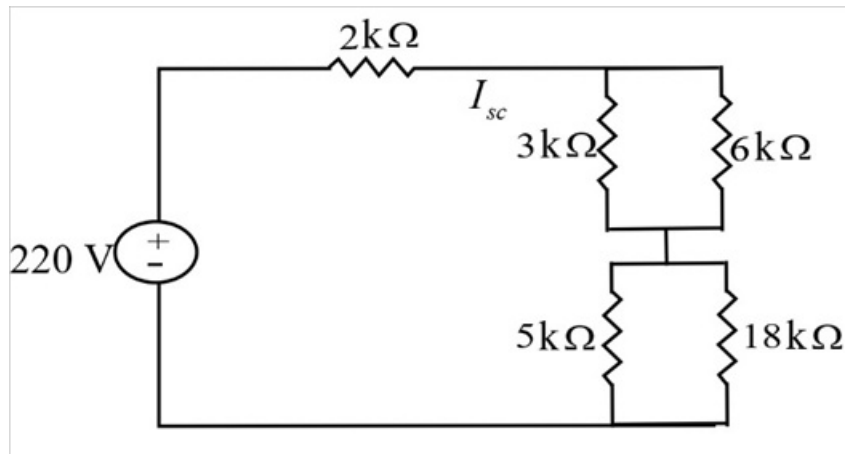


Figure 2

Step 7 of 12

Since, the resistance, $3\text{ k}\Omega \parallel 6\text{ k}\Omega$ and $5\text{ k}\Omega \parallel 18\text{ k}\Omega$, are in series.

The equivalent resistance Z , is given by,

$$\begin{aligned} Z &= (3\text{ k}\Omega \parallel 6\text{ k}\Omega) + (5\text{ k}\Omega \parallel 18\text{ k}\Omega) \\ &= \frac{(3)(6)}{3+6} + \frac{(5)(18)}{5+18} \\ &= 2 + 3.91 \\ &= 5.91\text{ k}\Omega \end{aligned}$$

Step 8 of 12

The following is the modified circuit diagram of Figure 2 as shown in Figure 3.

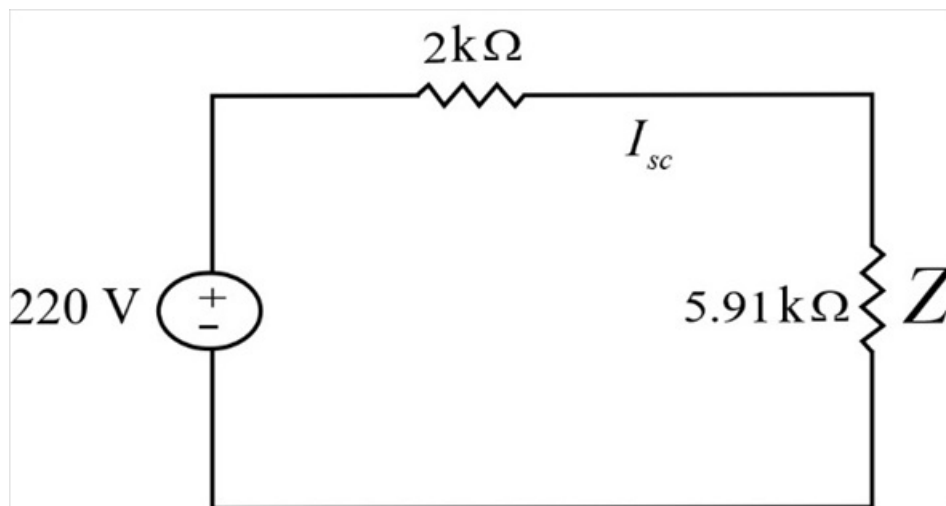


Figure 3

Step 9 of 12

Determine the short circuit current I_{sc} , that would flow when point a, and b are shorted as shown in Figure 3.

Apply KVL in Figure 3.

$$(2 + 5.91)I_{sc} = 220$$

$$I_{sc} = \frac{220}{7.91}$$

$$I_{sc} = 27.81 \text{ mA}$$

$$I_{sc} = 27.81 \text{ mA}$$

Step 10 of 12

Determine the open circuit voltage V_{oc} , across point a, and b using Figure 1.

$$V_{ab} = 5(i_1 - i_2) + 18(-i_2)$$

$$V_{ab} = 5i_1 - 23i_2$$

Here,

$$V_{ab} \text{ is same as } V_{oc}, \quad V_{ab} = V_{oc}.$$

Substitute 27.48 mA for i_1 , and 6.87 mA for i_2 .

$$V_{ab} = 5(27.48) - 23(6.87)$$

$$= 137.48 - 158.01$$

$$= -20.53 \text{ V}$$

$$|V_{ab}| = 20.53 \text{ V}$$

Step 11 of 12

Determine the resistor connected between terminal $a - b$, R_{Th} .

$$R_{Th} = \frac{V_{oc}}{I_{sc}}$$

$$= \frac{V_{ab}}{I_{sc}}$$

Here,

R_{Th} is the Thevenin resistance.

Substitute 20.53 V for $|V_{ab}|$, and 27.81 mA for I_{sc} .

$$R_{Th} = \frac{20.53}{27.81 \times 10^{-3}}$$

$$= 0.738 \text{ k}\Omega$$

$$R_{Th} = 0.738 \text{ k}\Omega$$

Therefore, the resistor connected between terminal $a - b$, R_{Th} is 0.738 kΩ.

Step 12 of 12

Determine the maximum absorb power by the resistor R_{Th} .

$$P_{\max} = \frac{v_{ab}^2}{4R_{Th}}$$

Substitute $0.738 \text{ k}\Omega$ for R_{Th} , and 20.53 V for $|v_{ab}|$.

$$\begin{aligned} P_{\max} &= \frac{(20.53)^2}{4(0.738 \times 10^3)} \\ &= \frac{421.48}{2952} \\ &= 0.143 \text{ W} \end{aligned}$$

$$P_{\max} = 0.143 \text{ W}$$

Therefore, the maximum absorb power by the resistor R_{Th} is $P_{\max} = 0.143 \text{ W}$.