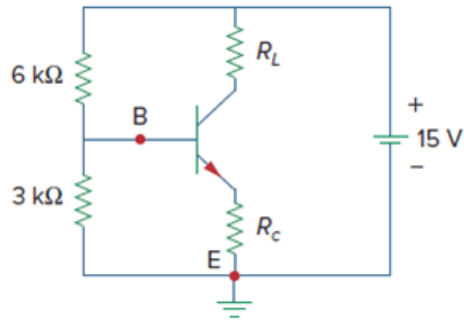


Problem


A common-emitter amplifier circuit is shown in Fig. 4.152. Obtain the Thevenin equivalent to the left of points *B* and *E*.

Figure. 4.152:



Step-by-step solution

Step 1 of 2

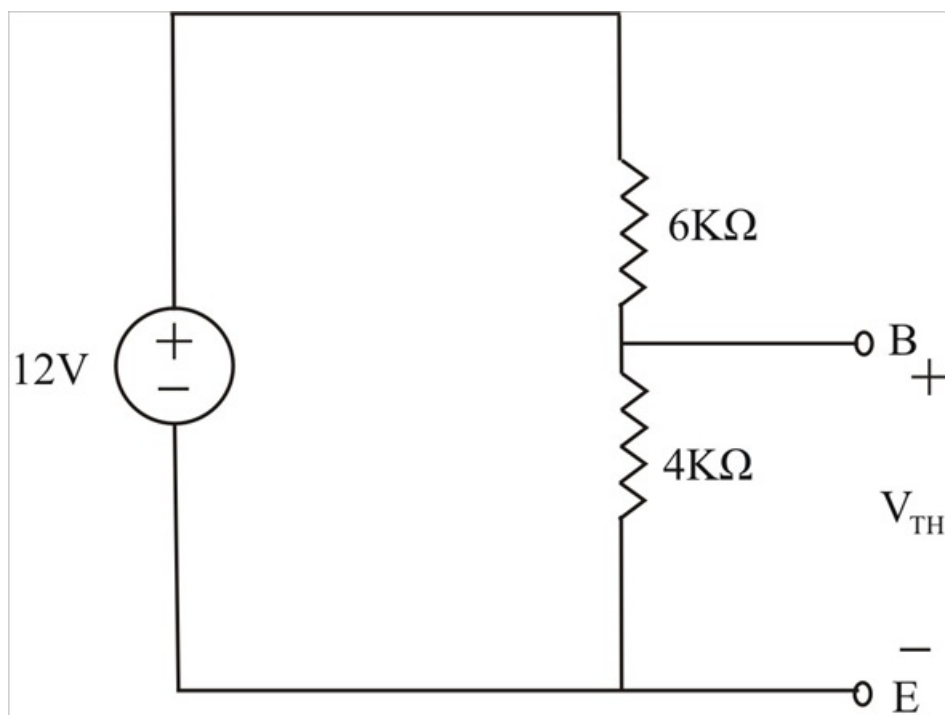

Step 2 of 2

$$R_{TH} = R_1 \parallel R_2 = 6 \parallel 4 = 2.4 \text{ K Ohms} .$$

$$V_{TH} = \left[\frac{R_2}{(R_1 + R_2)} \right] V_s = \left[\frac{4}{(6+4)} \right] [12] = 4.8 \text{ V} .$$