

Chapter 5, Problem 1RQ

Problem

The two input terminals of an op amp are labeled as:

- (a) high and low.
- (b) positive and negative.
- (c) inverting and noninverting.
- (d) differential and nondifferential.

Step-by-step solution

Step 1 of 1

(C) Inverting and non - Inverting.