

Chapter 5, Problem 2P

Problem

The open-loop gain of an op amp is 50,000. Calculate the output voltage when there are inputs of $+10\text{ }\mu\text{V}$ on the inverting terminal and $+20\text{ }\mu\text{V}$ on the noninverting terminal.

Step-by-step solution

Step 1 of 2

Write the expression for output voltage of op-amp.

$$\begin{aligned}v_o &= Av_d \\&= A(v_2 - v_1)\end{aligned}$$

Here,

A is the open loop voltage gain

v_1 is the inverting terminal voltage

v_2 is the noninverting terminal voltage

[Comments \(1\)](#)



Anonymous

v2 non inverting terminal

Step 2 of 2

Calculate the output voltage.

$$v_o = A(v_2 - v_1)$$

Substitute 50,000 for A , $10\text{ }\mu\text{V}$ for v_1 , and $20\text{ }\mu\text{V}$ for v_2 in the above equation.

$$\begin{aligned}v_o &= (50000)(20 \times 10^{-6} - 10 \times 10^{-6}) \\&= (50000)(10 \times 10^{-6}) \\&= 0.5\text{ V}\end{aligned}$$

Therefore, the output voltage, v_o is 0.5 V .