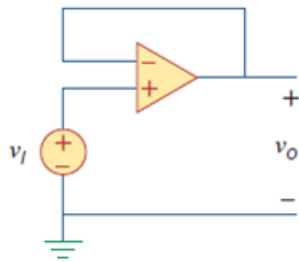


Problem

For the op amp circuit of Fig. 5.44, the op amp has an open-loop gain of 100,000, an input resistance of 10 k Ω , and an output resistance of 100 Ω . Find the voltage gain v_o/v_i using the nonideal model of the op amp.

Figure. 5.44:



Step-by-step solution

Step 1 of 5

Given that,

$$R_i = 10\text{ k}\Omega,$$

$$R_o = 100\Omega \text{ and}$$

$$A = 100,000.$$

Step 2 of 5

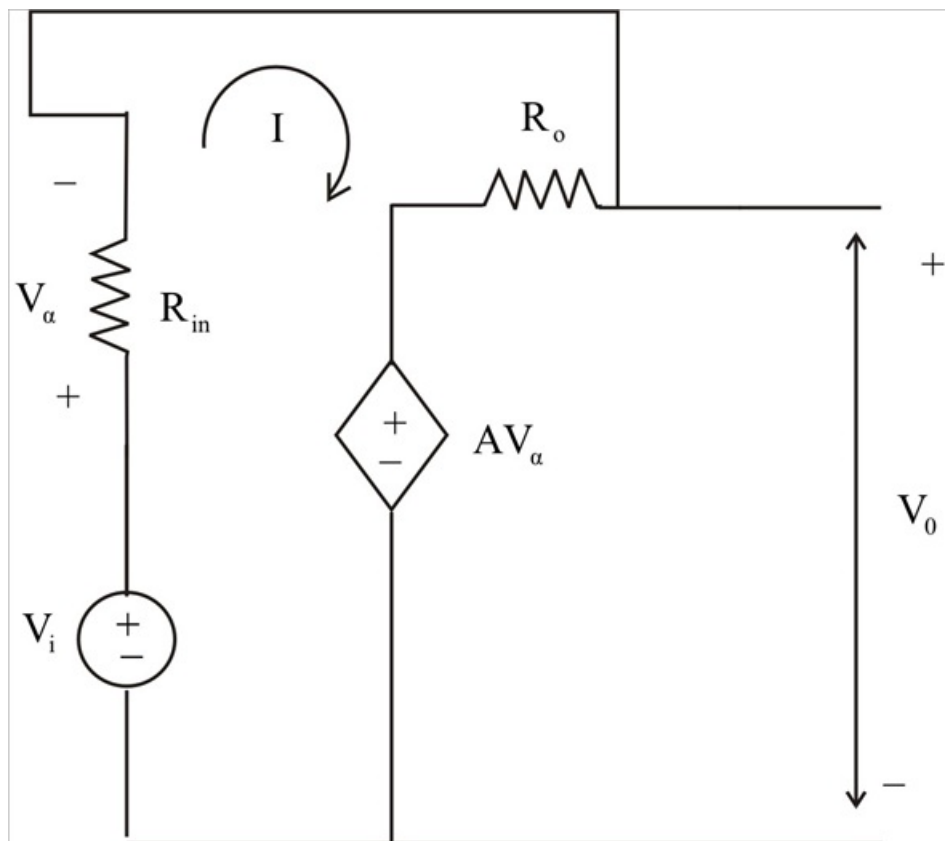


Fig-(a)

Step 3 of 5

From Fig-(a),

Applying KVL,

$$-V_i + AV_\alpha + (R_i + R_0)I = 0 \dots\dots\dots (1)$$

But,

$$V_\alpha = R_i I \dots\dots\dots (2)$$

From Equations-(1)

$$-V_i + (R_i + R_0 + R_i A)I = 0$$

$$I = \frac{V_i}{R_0 + (1 + A)R_i} \dots\dots\dots (3)$$

Step 4 of 5

Applying KVL to outer loop we get,

$$-AV_\alpha - R_0 I + V_0 = 0$$

$$V_0 = AV_\alpha + R_0 I$$

$$V_0 = (R_0 + R_i A)I \text{ (From Equations-(2))}$$

$$V_0 = \frac{(R_0 + R_i A)V_i}{R_0 + (1 + A)R_i} \text{ (From Equations-(3))}$$

Step 5 of 5

Therefore,

$$\frac{V_0}{V_i} = \frac{R_0 + R_i A}{R_0 + (1 + A)R_i}$$

$$\frac{V_0}{V_i} = \frac{100 + 10 \times 10^3 \times 10^5}{100 + (1 + 10^5) \times 10^4}$$

$$\frac{V_0}{V_i} \approx \frac{10^9}{(1 + 10^5) \times 10^4}$$

$$\boxed{\frac{V_0}{V_i} = 0.9999990}$$

[Comments \(1\)](#)



Anonymous

the correct answer is 0.999990 not 0.9999990.