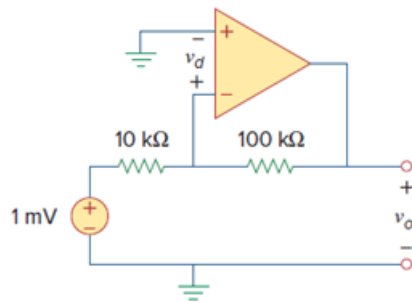


Problem

The op amp in Fig. 5.46 has $R_i = 100\text{ k}\Omega$, $R_o = 100\text{ }\Omega$, $A = 100,000$. Find the differential voltage v_d and the output voltage v_o .

Figure. 5.46:



Step-by-step solution

Step 1 of 5

Refer to circuit diagram in Figure 5.46 in the textbook.

Draw the equivalent circuit of the circuit shown in Figure 5.46.

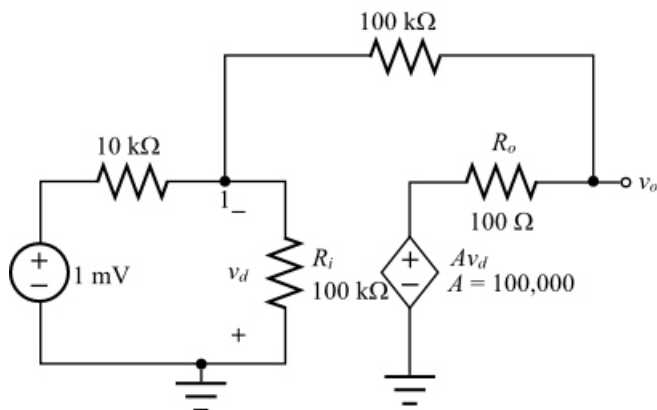


Figure 1

Step 2 of 5

From the circuit shown in Figure 1,

$$v_1 = -v_d$$

Apply Kirchhoff's current law at node 1.

$$\begin{aligned} \frac{v_1 - 1 \text{ mV}}{10 \text{ k}\Omega} + \frac{v_1}{100 \text{ k}\Omega} + \frac{v_1 - v_o}{100 \text{ k}\Omega} &= 0 \\ \frac{v_1}{10 \text{ k}\Omega} + \frac{v_1}{100 \text{ k}\Omega} + \frac{v_1}{100 \text{ k}\Omega} - \frac{v_o}{100 \text{ k}\Omega} &= \frac{1 \text{ mV}}{10 \text{ k}\Omega} \\ \left(\frac{1}{10 \text{ k}\Omega} + \frac{1}{100 \text{ k}\Omega} + \frac{1}{100 \text{ k}\Omega} \right) v_1 - \frac{v_o}{100 \text{ k}\Omega} &= \frac{1 \text{ mV}}{10 \text{ k}\Omega} \\ \left(\frac{10+1+1}{100 \text{ k}\Omega} \right) v_1 - \frac{v_o}{100 \text{ k}\Omega} &= \frac{1 \text{ mV}}{10 \text{ k}\Omega} \end{aligned}$$

$$12v_1 - v_o = 10 \text{ mV}$$

Substitute $-v_d$ for v_1 in the equation.

$$-12v_d - v_o = 10 \text{ mV} \dots\dots (1)$$

Step 3 of 5

Apply Kirchhoff's current law at node v_o .

$$\frac{v_o - v_1}{100 \text{ k}\Omega} + \frac{v_o - Av_d}{100 \Omega} = 0$$

Substitute $-v_d$ for v_1 in the equation.

$$\begin{aligned} \frac{v_o + v_d}{100 \text{ k}\Omega} + \frac{v_o - Av_d}{100 \Omega} &= 0 \\ \frac{v_o}{100 \text{ k}\Omega} + \frac{v_o}{100 \Omega} + \frac{v_d}{100 \text{ k}\Omega} - \frac{100000v_d}{100 \Omega} &= 0 \quad (A = 100,000) \\ \left(\frac{1}{100 \text{ k}\Omega} + \frac{1}{100 \Omega} \right) v_o + \left(\frac{1}{100 \text{ k}\Omega} - \frac{100000}{100 \Omega} \right) v_d &= 0 \\ \left(\frac{1+1000}{100 \text{ k}\Omega} \right) v_o + \left(\frac{1-10^8}{100 \text{ k}\Omega} \right) v_d &= 0 \\ 1001v_o - 99999999v_d &= 0 \\ 1001v_o &= 99999999v_d \\ v_o &= 99900.099v_d \dots\dots (2) \end{aligned}$$

Step 4 of 5

Recall equation (1).

$$-12v_d - v_o = 10 \text{ mV}$$

Substitute $99900.099v_d$ for v_o in the equation.

$$\begin{aligned} -12v_d - 99900.099v_d &= 10 \text{ mV} \\ -99912.099v_d &= 10 \text{ mV} \\ v_d &= -100 \text{ nV} \end{aligned}$$

Therefore, the differential voltage, v_d is -100 nV .

Step 5 of 5

Calculate the output voltage.

Recall equation (2).

$$v_o = 99900.099v_d$$

Substitute -100 nV for v_d in the equation.

$$\begin{aligned} v_o &= (99900.099)(-100 \text{ nV}) \\ &= -9.99 \text{ mV} \\ &= -10 \text{ mV} \end{aligned}$$

Therefore, the output voltage, v_o is $\boxed{-10 \text{ mV}}$.