

Problem

Design a difference amplifier with gain 7.5.

Step-by-step solution

Step 1 of 4

Draw the difference amplifier circuit diagram as shown in Figure 1.

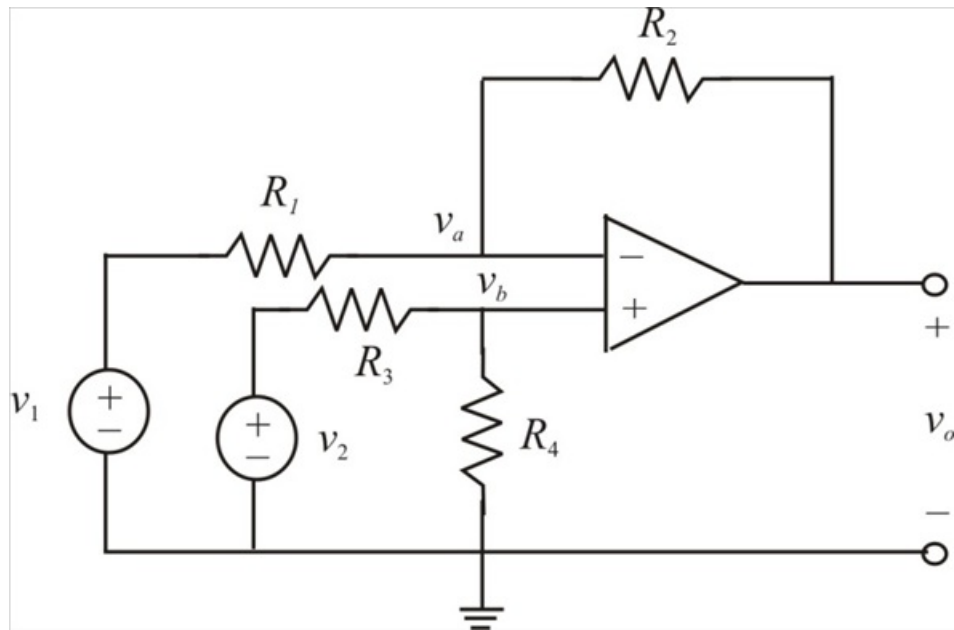


Figure 1

Step 2 of 4

The gain of the difference amplifier = 7.5

The circuit is labeled as shown in Figure 2.

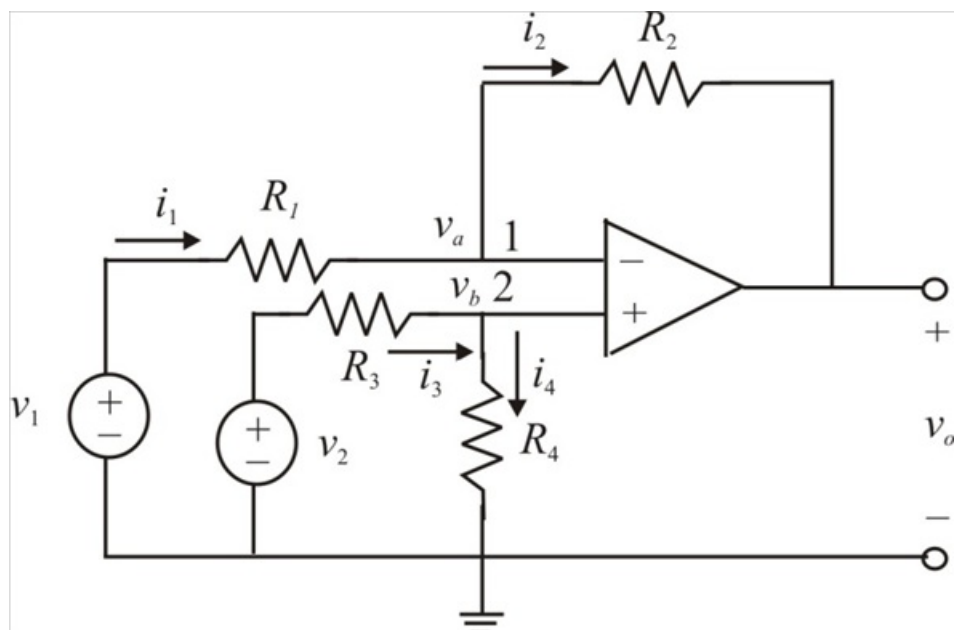


Figure 2

Applying Kirchhoff's current law to node 1,

$$i_1 = i_2$$

$$\frac{v_1 - v_a}{R_1} = \frac{v_a - v_o}{R_2}$$

$$v_o = \left(\frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1$$

Therefore $v_o = \left(\frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1 \dots\dots (1)$

Applying Kirchhoff's current law to node 2,

$$i_3 = i_4$$

$$\frac{v_2 - v_b}{R_3} = \frac{v_b - 0}{R_4}$$

$$v_b = \frac{R_4}{R_3 + R_4} v_2$$

Therefore $v_b = \frac{R_4}{R_3 + R_4} v_2 \dots\dots (2)$

But $v_a = v_b$ for an ideal op amp, substituting the equation (2) in equation (1), we get

$$\begin{aligned} v_o &= \left(\frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1 \\ &= \frac{R_2 (1 + R_1 / R_2)}{R_1 (1 + R_3 / R_4)} v_2 - \frac{R_2}{R_1} v_1 \end{aligned}$$

Since a difference amplifier must reject a signal common to the two inputs, the amplifier must have the property that $v_o = 0$ when $v_1 = v_2$.

This property exist when

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

When the op amp circuit is a difference amplifier v_o becomes,

$$v_o = \frac{R_2}{R_1} (v_2 - v_1)$$

Hence the gain is

$$\begin{aligned} \frac{v_o}{v_2 - v_1} &= \frac{R_2}{R_1} = 7.5 \\ R_2 &= 7.5 R_1 \end{aligned}$$

But

$$\begin{aligned} \frac{R_1}{R_2} &= \frac{R_3}{R_4} = \frac{1}{7.5} \\ R_4 &= 7.5 R_3 \end{aligned}$$

If $R_1 = 20 \text{ k}\Omega$, then $R_2 = 150 \text{ k}\Omega$

If $R_3 = 20 \text{ k}\Omega$, then $R_4 = 150 \text{ k}\Omega$

Therefore the resistance R_1 is $20 \text{ k}\Omega$.

Therefore the resistance R_2 is $150 \text{ k}\Omega$.

Therefore the resistance R_3 is $20 \text{ k}\Omega$.

Therefore the resistance R_4 is $150 \text{ k}\Omega$.

The desired difference amplifier circuit diagram as shown in Figure 3.

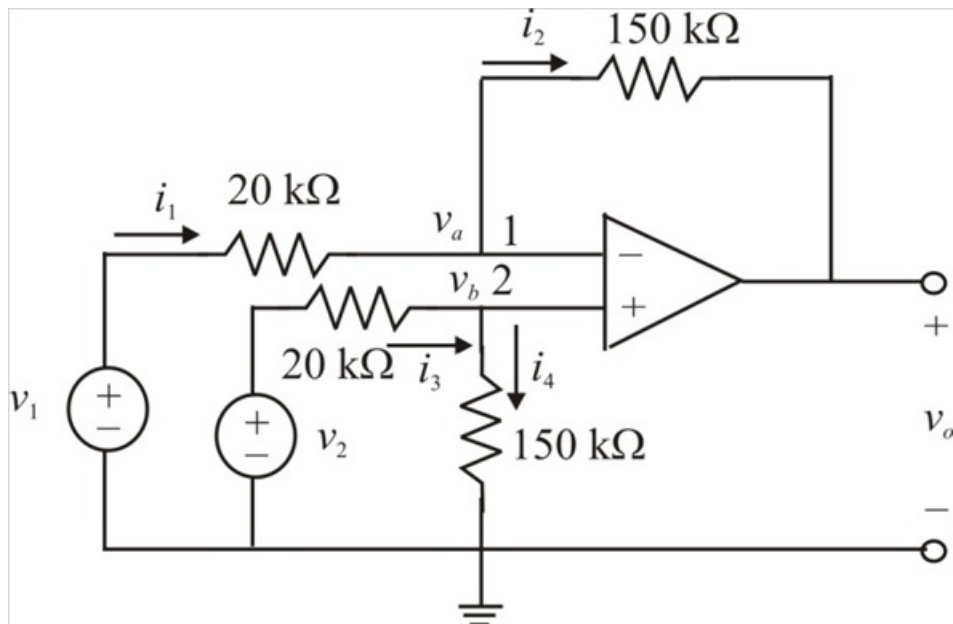


Figure 3