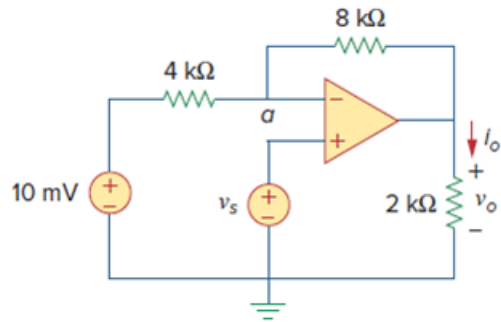


Problem

Refer to Fig. 5.41. If $v_s = 8 \text{ mV}$, voltage v_a is:

- (a) -8 mV
- (b) 0 mV
- (c) $10/3 \text{ mV}$
- (d) 8 mV

Figure 5.41:



Step-by-step solution

Step 1 of 1

Answer: (d)

8 mV