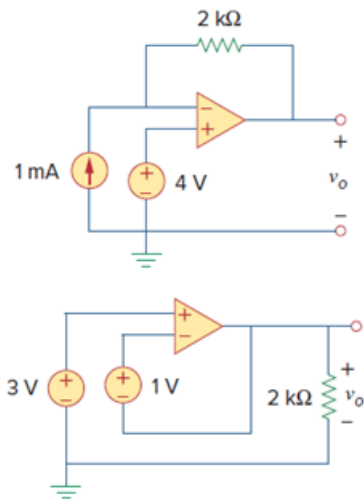


Problem

Determine v_o for each of the op amp circuits in Fig. 5.48.

Figure 5.48:



Step-by-step solution

Step 1 of 4

The following is the given circuit diagram:

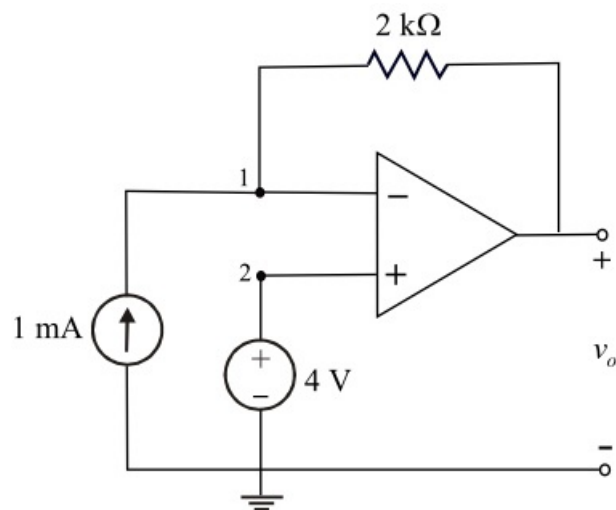


Figure 1

Step 2 of 4

The voltage at non inverting terminal is,

$$v_2 = 4 \text{ V}$$

Since the given op amp is ideal op amp. Hence,

$$v_1 = v_2 = 4 \text{ V}$$

Apply Kirchhoff's current law at node 1.

$$\frac{v_1 - v_o}{2 \text{ k}} - 1 \times 10^{-3} = 0$$

$$\frac{v_1 - v_o}{2 \text{ k}} = 1 \times 10^{-3}$$

$$v_1 - v_o = 2$$

$$v_o = v_1 - 2$$

$$= 4 - 2$$

$$= 2 \text{ V}$$

Therefore, the output voltage, v_o is **2 V**.

Step 3 of 4

The following is the given circuit diagram:

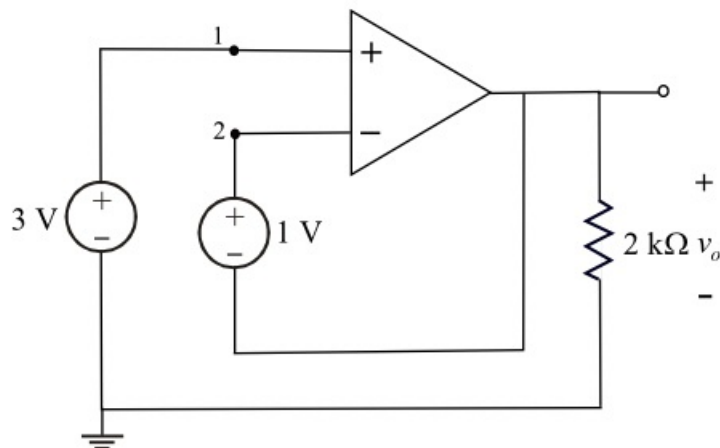


Figure 2

Step 4 of 4

From the Figure 2, the non-inverting input voltage is,

$$v_1 = 3 \text{ V}$$

The inverting input voltage and non-inverting input voltages are same because the given op amp is ideal.

That is, $v_1 = v_2 = 3 \text{ V}$

Apply Kirchhoff's voltage law to the Figure 2.

$$v_2 - v_o = 1 \text{ V} \dots\dots (1)$$

Substitute equation $v_2 = 3 \text{ V}$ in equation (1).

$$3 - v_o = 1$$

$$v_o = 3 - 1$$

$$v_o = 2 \text{ V}$$

Therefore, the output voltage, v_o is **2 V**.