

Problem

Which of these amplifiers is used in a digital-to-analog converter?

- (a) noninverter
- (b) voltage follower
- (c) summer
- (d) difference amplifier

Step-by-step solution**Step 1 of 4**

The main purpose of non-inverter is to improve the gain and provide 180° phase shift, which indicates the gain of the circuit is inversion of input voltage. So, it is not used in digital-to-analog converter.

Thus, option a is wrong.

Step 2 of 4

The purpose of voltage follower is to provide unity voltage gain. So, it is not used in digital-to-analog converter.

Thus, option b is wrong.

Step 3 of 4

The difference amplifier is used to provide the difference of voltage between the inverting and non-inverting terminals. So, it is not used in digital-to-analog converter.

Thus, option d is wrong.

Step 4 of 4

The summer amplifier provides the weighted sum of the input which means it combines several input to produce the output. So, it is used in digital-to-analog converter.

Thus, the correct answer is **Option (c)**.