

Problem

Difference amplifiers are used in (please check all that apply):

- (a) instrumentation amplifiers
- (b) voltage followers
- (c) voltage regulators
- (d) buffers
- (e) summing amplifiers
- (f) subtracting amplifiers

Step-by-step solution**Step 1** of 2

The instrumentation amplifier is an extension of the difference amplifier in that it amplifies the difference between its input signals.

Therefore, option (a) is correct.

Step 2 of 2

The difference amplifier is also known as the subtractor.

Therefore, option (f) is correct.

Thus the difference amplifiers are used in instrumentation amplifiers and subtracting amplifiers.

Therefore, the correct options are *a, f*.