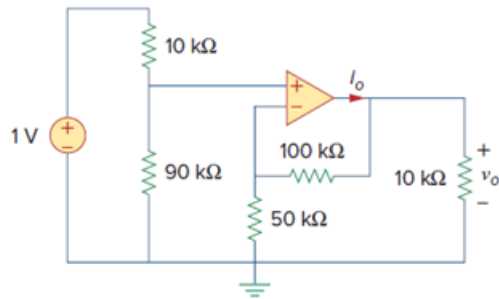


Problem

Find v_o and i_o in the circuit of Fig. 5.52.

Figure. 5.52:




Step-by-step solution

Step 1 of 4

Refer to circuit diagram in Figure 5.52 in the textbook.

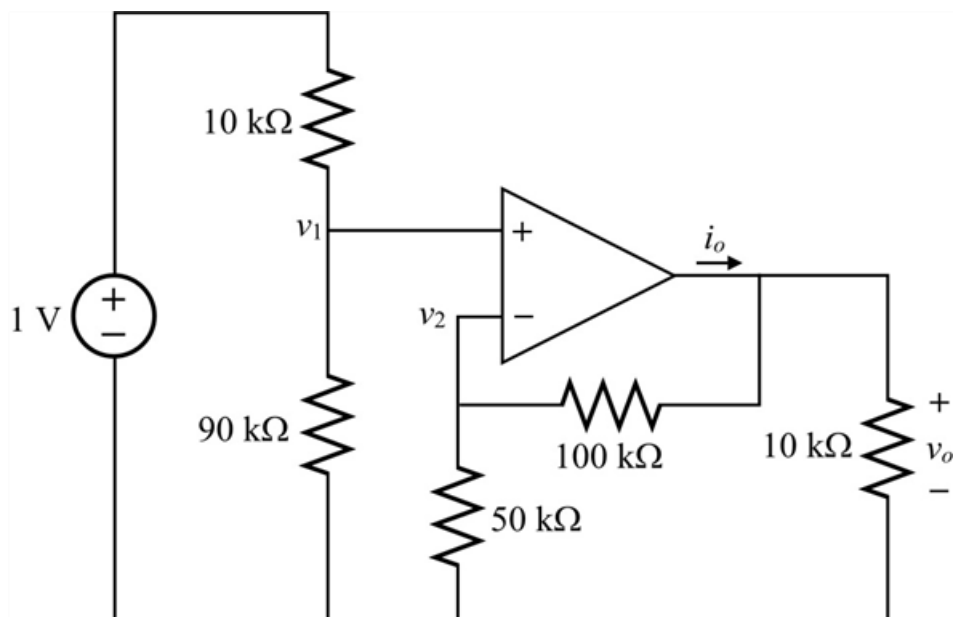Draw the circuit diagram with node notations.



Step 2 of 4

Apply Kirchhoff's current law at node v_1 .

$$\begin{aligned}\frac{v_1 - 1 \text{ V}}{10 \text{ k}\Omega} + \frac{v_1}{90 \text{ k}\Omega} &= 0 \\ \left(\frac{1}{10 \text{ k}\Omega} + \frac{1}{90 \text{ k}\Omega} \right) v_1 &= \frac{1 \text{ V}}{10 \text{ k}\Omega} \\ \left(\frac{9+1}{90 \text{ k}\Omega} \right) v_1 &= \frac{1 \text{ V}}{10 \text{ k}\Omega} \\ v_1 &= \left(\frac{1 \text{ V}}{10 \text{ k}\Omega} \right) \left(\frac{90 \text{ k}\Omega}{10} \right) \\ &= 0.9 \text{ V}\end{aligned}$$

It is known that, the voltages at inverting and non-inverting terminals of the op-amp are same for ideal op-amp.

$$\begin{aligned}v_1 &= v_2 \\ &= 0.9 \text{ V}\end{aligned}$$

Step 3 of 4

Apply Kirchhoff's current law at node v_2 .

$$\begin{aligned}\frac{v_2}{50 \text{ k}\Omega} + \frac{v_2 - v_o}{100 \text{ k}\Omega} &= 0 \\ \frac{v_o}{100 \text{ k}\Omega} &= \left(\frac{1}{50 \text{ k}\Omega} + \frac{1}{100 \text{ k}\Omega} \right) v_2 \\ \frac{v_o}{100 \text{ k}\Omega} &= \left(\frac{2+1}{100 \text{ k}\Omega} \right) v_2 \\ v_o &= 3v_2\end{aligned}$$

Substitute 0.9 V for v_2 .

$$\begin{aligned}v_o &= 3(0.9 \text{ V}) \\ &= 2.7 \text{ V}\end{aligned}$$

Therefore, the value of output voltage, v_o is $\boxed{2.7 \text{ V}}$.

Step 4 of 4

Apply Kirchhoff's current law at node v_o .

$$i_o = \frac{v_o - v_2}{100 \text{ k}\Omega} + \frac{v_o}{10 \text{ k}\Omega}$$

Substitute 2.7 V for v_o and 0.9 V for v_2 .

$$\begin{aligned}i_o &= \frac{2.7 \text{ V} - 0.9 \text{ V}}{100 \text{ k}\Omega} + \frac{2.7 \text{ V}}{10 \text{ k}\Omega} \\ &= \frac{1.8 \text{ V} + 27 \text{ V}}{100 \text{ k}\Omega} \\ &= \frac{28.8 \text{ V}}{100 \text{ k}\Omega} \\ &= 0.288 \text{ mA}\end{aligned}$$

Therefore, the current, i_o is $\boxed{0.288 \text{ mA}}$.