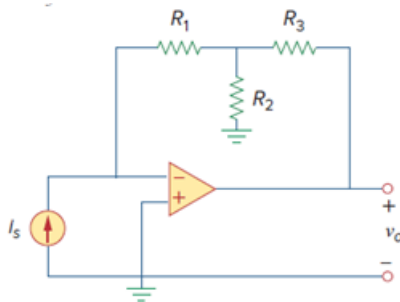


Problem

(a) Determine the ratio v_o/i_s in the op amp circuit of Fig. 5.54.

(b) Evaluate the ratio for $R_1 = 20 \text{ k}\Omega$, $R_2 = 25 \text{ k}\Omega$, $R_3 = 40 \text{ k}\Omega$.

Figure 5.54:



Step-by-step solution

Step 1 of 3

(a)

Let V_1 be the voltage at the node where the three resistors meet.

Applying KVL, at this node gives,

$$i_s = \frac{V_1}{R_2} + \frac{V_1 - V_o}{R_3}$$

$$i_s = V_1 \left[\frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{V_o}{R_3} \dots \dots \dots (1)$$

At the inverting terminal,

$$i_s = \frac{0 - V_1}{R_1}$$

$$V_1 = -i_s R_1 \dots \dots \dots (2)$$

[Comments \(1\)](#)

☐

Anonymous

Applying K[C]L at this node...

Step 2 of 3

Combining (1) and (2) leads to,

$$i_s \left[1 + \frac{R_1}{R_2} + \frac{R_1}{R_3} \right] = \frac{-V_o}{R_3}$$

$$\boxed{\frac{V_o}{i_s} = - \left[R_1 + R_3 + \frac{R_1 R_3}{R_2} \right]}$$

Step 3 of 3

(b)

Given that,

$$R_1 = 20\text{k}\Omega,$$

$$R_2 = 25\text{k}\Omega \text{ and}$$

$$R_3 = 40\text{k}\Omega.$$

Therefore,

$$\frac{V_0}{i_s} = - \left[R_1 + R_3 + \frac{R_1 R_3}{R_2} \right]$$

$$\frac{V_0}{i_s} = - \left[20 \times 10^3 + 40 \times 10^3 + \frac{20 \times 10^3 \times 40 \times 10^3}{25 \times 10^3} \right]$$

$$\boxed{\frac{V_0}{i_s} = -92\text{k}\Omega}$$