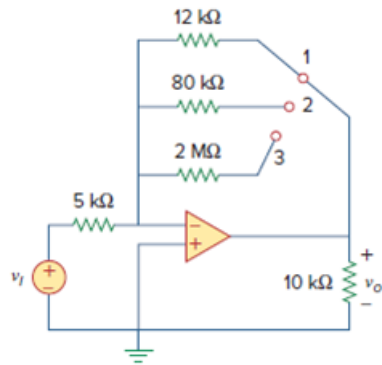


Problem

Calculate the gain v_o/v_i when the switch in Fig. 5.56 is in:

- (a) position 1
- (b) position 2
- (c) position 3.

Figure. 5.56:



Step-by-step solution


Step 1 of 6

(a)

Refer to Figure 5.56P in the textbook.

Consider the switch is in position 1.

Draw the following Figure 1.

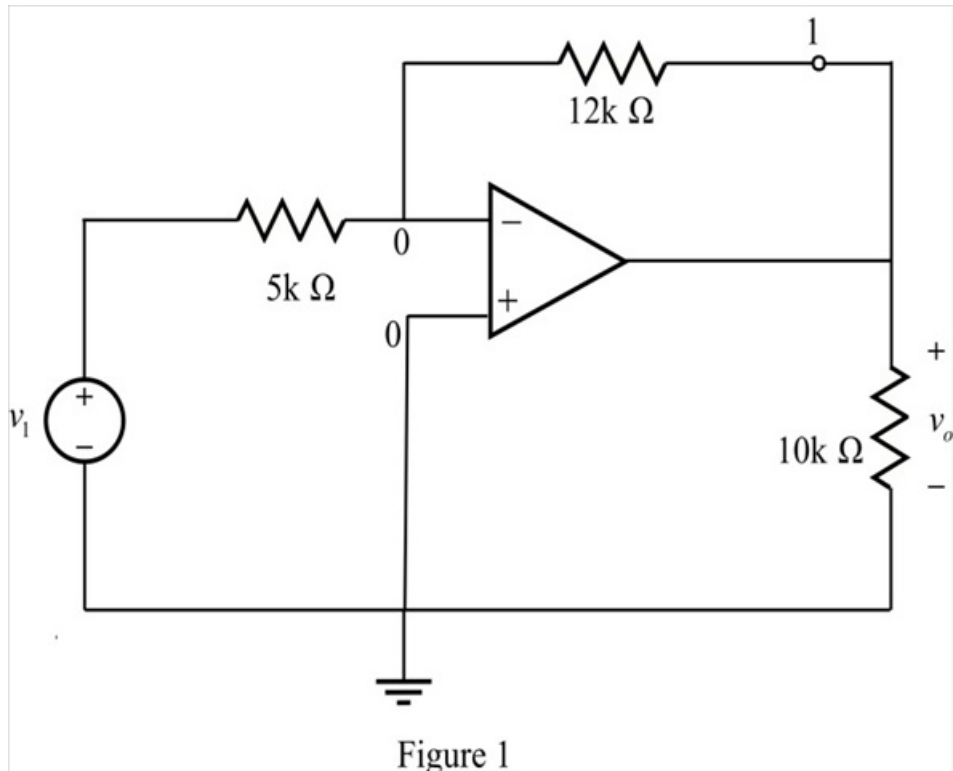

Step 2 of 6

Determine the ratio of $\frac{v_o}{v_i}$.

Apply Kirchhoff's current law at inverting terminal.

$$\frac{0 - v_i}{5 \text{ k}\Omega} + \frac{0 - v_o}{12 \text{ k}\Omega} = 0$$

$$-\frac{v_i}{5 \text{ k}\Omega} + \frac{-v_o}{12 \text{ k}\Omega} = 0$$

$$-\frac{v_i}{5 \text{ k}\Omega} = \frac{v_o}{12 \text{ k}\Omega}$$

$$v_o = -\frac{12}{5} v_i$$

$$v_o = -2.4 v_i$$

$$\frac{v_o}{v_i} = -2.4$$


Therefore, the ratio of $\frac{v_o}{v_i}$ in position 1 is -2.4.

Step 3 of 6

(b)

Consider the switch is in position 2.

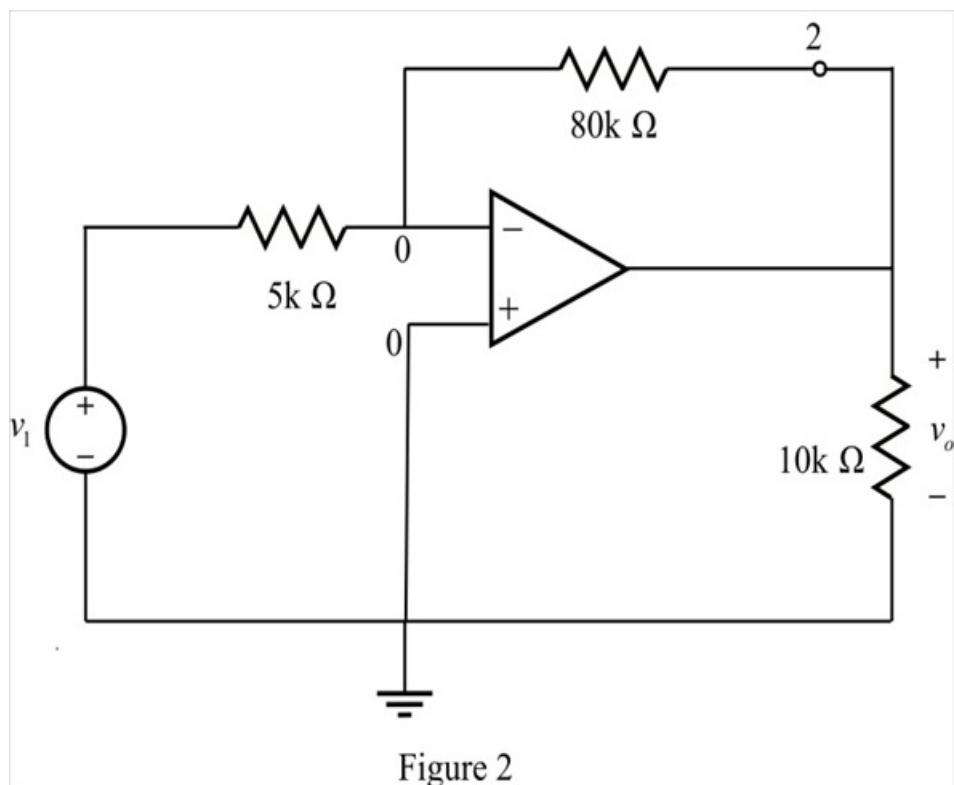Draw the modified circuit as shown in Figure 2.



Step 4 of 6

Determine the ratio of $\frac{v_o}{v_i}$.

Apply Kirchhoff's current law at inverting terminal.

$$\frac{0 - v_i}{5 \text{ k}\Omega} + \frac{0 - v_o}{80 \text{ k}\Omega} = 0$$

$$-\frac{v_i}{5 \text{ k}\Omega} + \frac{-v_o}{80 \text{ k}\Omega} = 0$$

$$-\frac{v_i}{5 \text{ k}\Omega} = \frac{v_o}{80 \text{ k}\Omega}$$

$$v_o = -\frac{80}{5} v_i$$

$$v_o = -16v_i$$

$$\frac{v_o}{v_i} = -16$$


Therefore, the ratio of $\frac{v_o}{v_i}$ in position 2 is -16.

Step 5 of 6

(c)

Consider the switch is in position 3.

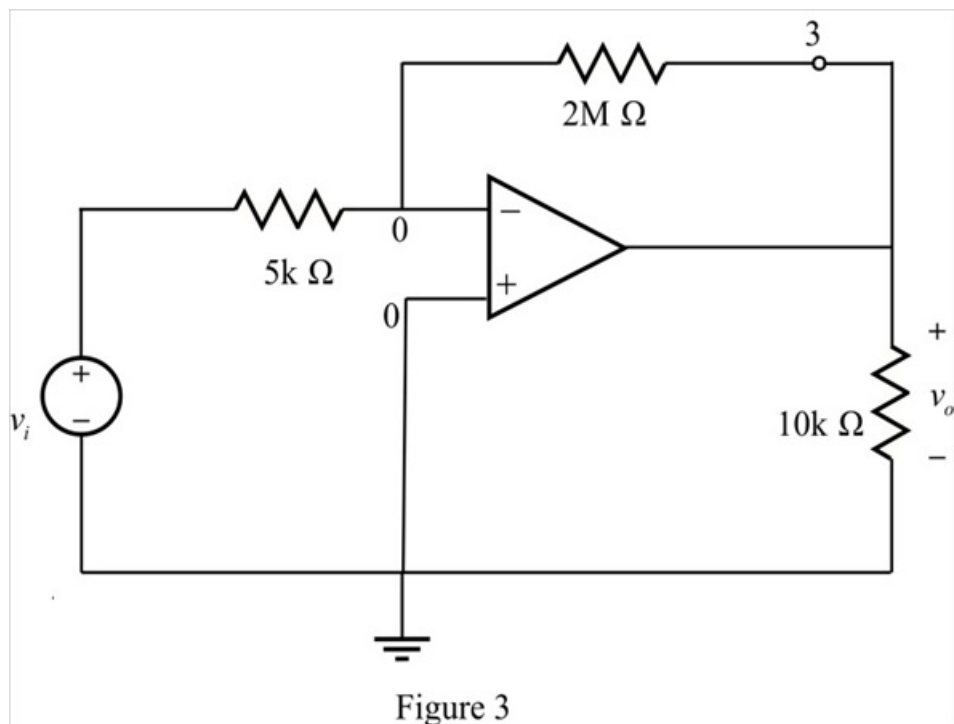Draw the modified circuit as shown in Figure 3.



Step 6 of 6

Determine the ratio of $\frac{v_o}{v_i}$.

Apply Kirchhoff's current law at inverting terminal.

$$\frac{0 - v_i}{5 \text{ k}\Omega} + \frac{0 - v_o}{2000 \text{ k}\Omega} = 0$$

$$-\frac{v_i}{5 \text{ k}\Omega} + \frac{-v_o}{2000 \text{ k}\Omega} = 0$$

$$-\frac{v_i}{5 \text{ k}\Omega} = \frac{v_o}{2000 \text{ k}\Omega}$$

$$v_o = -\frac{2000}{5} v_i$$

$$v_o = -400 v_i$$

$$\frac{v_o}{v_i} = -400$$

Therefore, the ratio of $\frac{v_o}{v_i}$ in position 3 is -400.