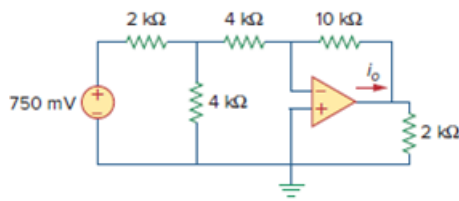


Problem

Determine i_o in the circuit of Fig. 5.58.

Figure 5.58:



Step-by-step solution

Step 1 of 5

Draw the circuit diagram as shown in Figure 1.

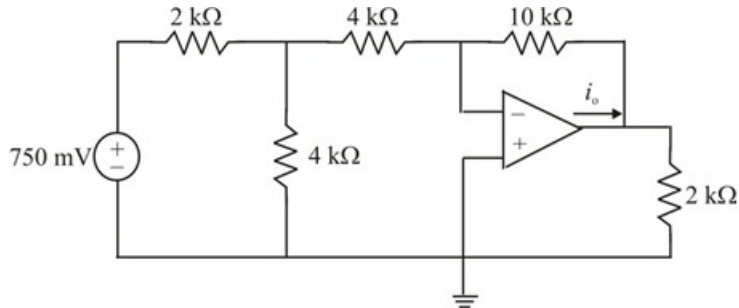


Figure 1

Step 2 of 5

The circuit is labeled as shown in Figure 2.

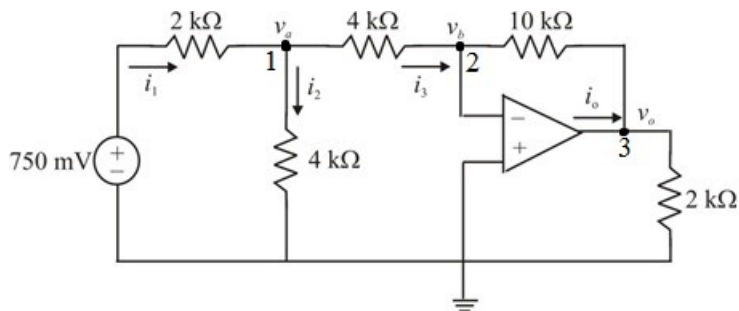


Figure 2

Step 3 of 5

Applying Kirchhoff's current law to node 1.

$$i_1 = i_2 + i_3$$

$$\left[\frac{(750 \times 10^{-3}) - v_a}{2} \right] = \left(\frac{v_a - 0}{4} \right) + \left(\frac{v_a - v_b}{4} \right)$$

$$1.5 - 2v_a = v_a + v_a - v_b$$

$$4v_a - v_b = 1.5$$

Therefore,

$$4v_a - v_b = 1.5 \dots\dots (1)$$

But, $v_b = 0$ since, non-inverting terminal is grounded.

Substitute 0 for v_b in equation (1).

$$4v_a - 0 = 1.5$$

$$v_a = 0.375 \text{ A}$$

Therefore, $v_a = 0.375 \text{ V}$

Apply Kirchhoff's current law at node 2.

$$i_3 = i_o$$

$$\frac{v_a - v_b}{4} = \frac{v_b - v_o}{10}$$

$$5v_a - 5v_b = 2v_b - 2v_o$$

$$2v_o = 7v_b - 5v_a$$

Therefore,

$$2v_o = 7v_b - 5v_a \dots\dots (2)$$

Step 4 of 5

But, $v_b = 0$ since non-inverting terminal is grounded.

Substitute 0 for v_b in equation (2).

$$\begin{aligned} 2v_o &= 7v_b - 5v_a \\ &= 7(0) - 5(0.375) \end{aligned}$$

$$v_o = -0.9375 \text{ V}$$

Step 5 of 5

Determine current i_o .

Apply Nodal analysis at node-3.

$$i_o = \frac{v_o - v_b}{10 \times 10^3} + \frac{v_o - 0}{2 \times 10^3}$$

But, $v_b = 0$ since non-inverting terminal is grounded.

Substitute 0 for v_b .

$$i_o = \frac{v_o}{10 \times 10^3} + \frac{v_o}{2 \times 10^3}$$

Substitute -0.9375 for v_o .

$$\begin{aligned} i_o &= \frac{-0.9375}{10 \times 10^3} + \frac{-0.9375}{2 \times 10^3} \\ &= -0.5625 \times 10^{-3} \\ &= -562.5 \mu\text{A} \end{aligned}$$

Therefore the current i_o is $-562.5 \mu\text{A}$.