

Problem

Design an inverting amplifier with a gain of -15.

Step-by-step solution

Step 1 of 1

$$A_v = \frac{-R_F}{R_i} = -15 .$$

$$\text{If } R_i = 10\text{ K}\Omega ,$$

$$\text{Then, } R_F = 150\text{ K}\Omega .$$