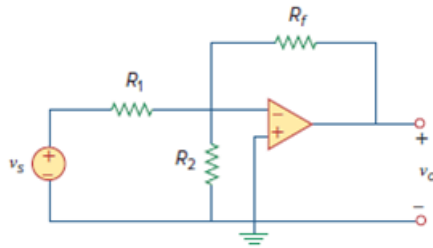


## Problem

For the op amp circuit in Fig. 5.61, find the voltage gain  $v_o/v_s$ .

**Figure. 5.61:**



## Step-by-step solution

## Step 1 of 1

At the inverting terminal,  $V = 0\text{V}$  So that KVL gives,

$$\frac{V_s - 0}{R_1} = \frac{0}{R_2} + \frac{0 - V_o}{R_f}$$

$$\therefore \boxed{\frac{V_o}{V_s} = -\frac{R_f}{R_1}}$$

[Comments \(1\)](#)



**Anonymous**

KCL not KVL