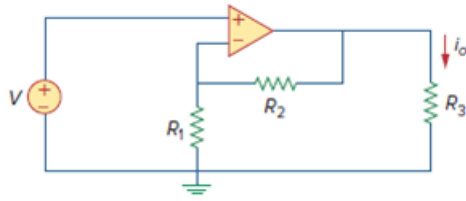


Problem

Using Fig. 5.64, design a problem to help other students better understand noninverting op amps.


Figure. 5.64:



Step-by-step solution


Step 1 of 5

Considering the non inverting OP amps

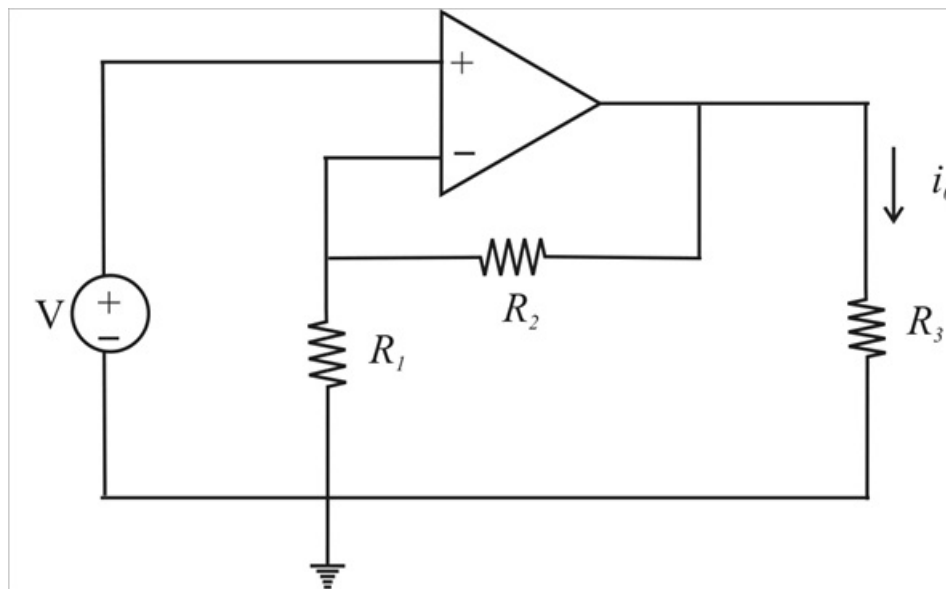

Step 2 of 5

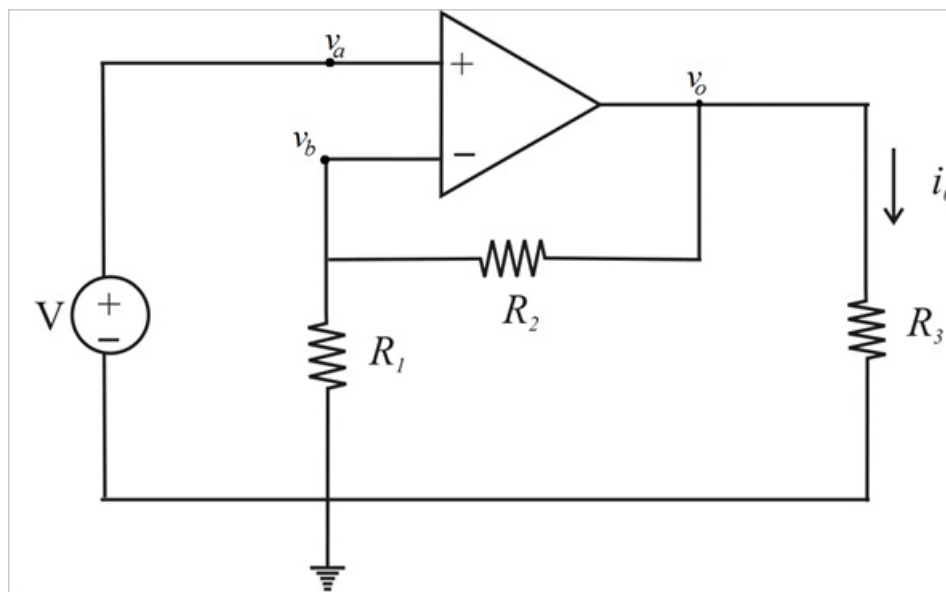For the analysis purpose the above circuit is modified as follows



Step 3 of 5

From the circuit $v_a = V$

OP amp is ideal so

$$v_a = v_b$$

$$\therefore v_b = V$$

Step 4 of 5

By applying KCL at node v_b

$$\frac{v_b}{R_1} + \frac{v_b - v_o}{R_2} = 0$$

$$v_b \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_o}{R_2}$$

$$V \left(\frac{R_1 + R_2}{R_1 R_2} \right) = \frac{v_o}{R_2}$$

$$v_o = V \left(\frac{R_1 + R_2}{R_1} \right)$$

Step 5 of 5

But $i_o = \frac{v_o}{R_3}$

$$i_o = \frac{V \left(\frac{R_1 + R_2}{R_1} \right)}{R_3}$$

$$\therefore i_o = V \left(\frac{R_1 + R_2}{R_1 R_3} \right) \text{ A}$$