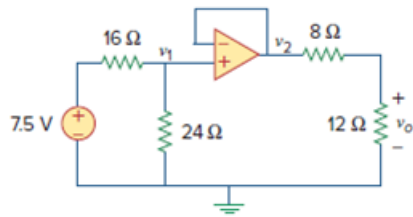


Problem

Find v_o in the op amp circuit of Fig. 5.65.

Figure. 5.65:



Step-by-step solution

Step 1 of 3

Draw the circuit diagram as shown in Figure 1.

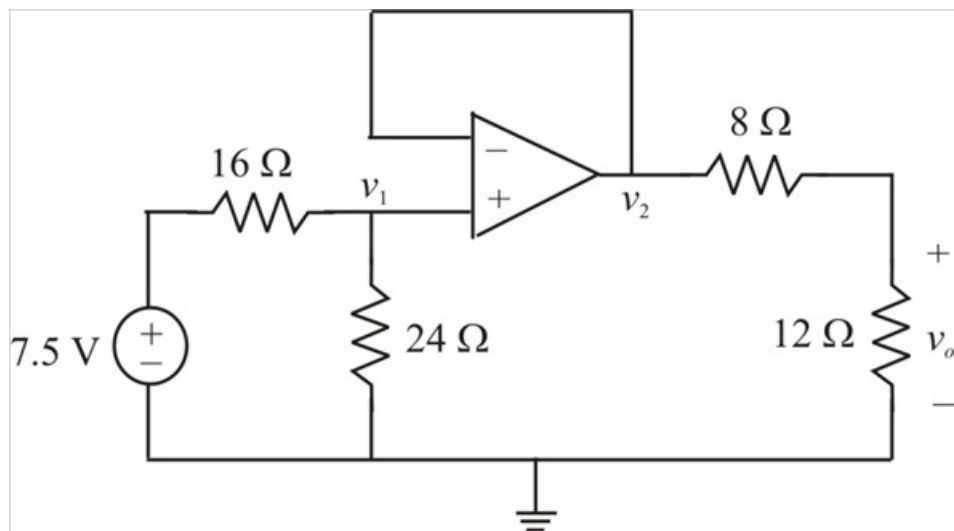


Figure 1

Step 2 of 3

The circuit is labeled as shown in Figure 2.

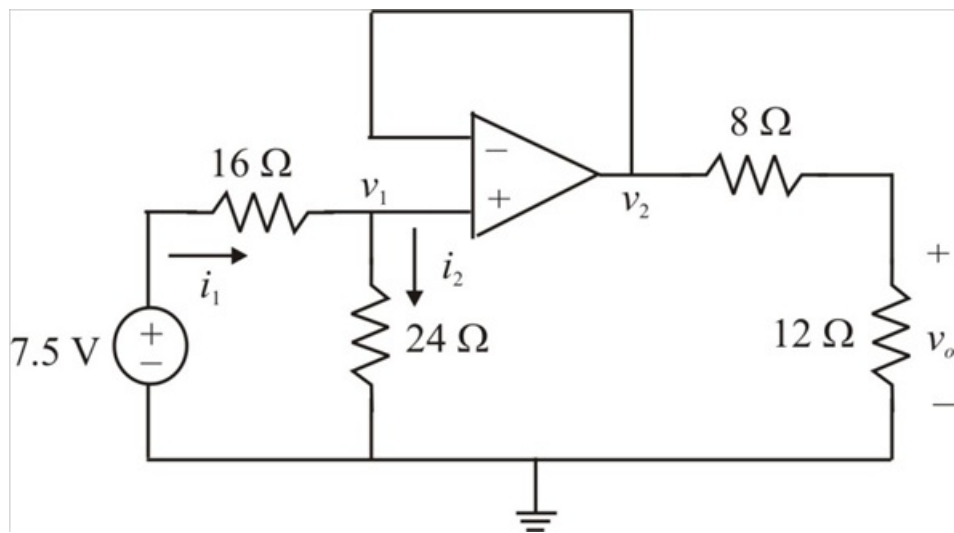


Figure 2

Step 3 of 3

Applying Kirchhoff's current law to node 1,

$$i_1 = i_2$$

$$\frac{7.5 - v_1}{16} = \frac{v_1 - 0}{24}$$

$$22.5 - 3v_1 = 2v_1$$

$$5v_1 = 22.5$$

$$v_1 = 4.5 \text{ V}$$

But, $v_1 = v_2$ for an ideal op amp

Therefore voltage $v_2 = 4.5 \text{ V}$

Applying voltage division,

$$\begin{aligned} v_o &= \frac{12}{12+8}(v_2) \\ &= \frac{12}{12+8}(4.5) \\ &= 2.7 \text{ V} \end{aligned}$$

Therefore the voltage v_o is 2.7 V.