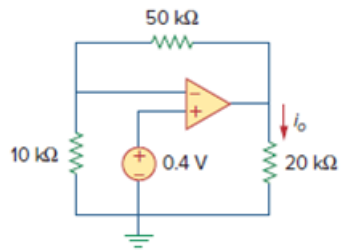


Problem

Find i_o in the op amp circuit of Fig. 5.66.

Figure. 5.66:



Step-by-step solution

Step 1 of 4

Given circuit is,

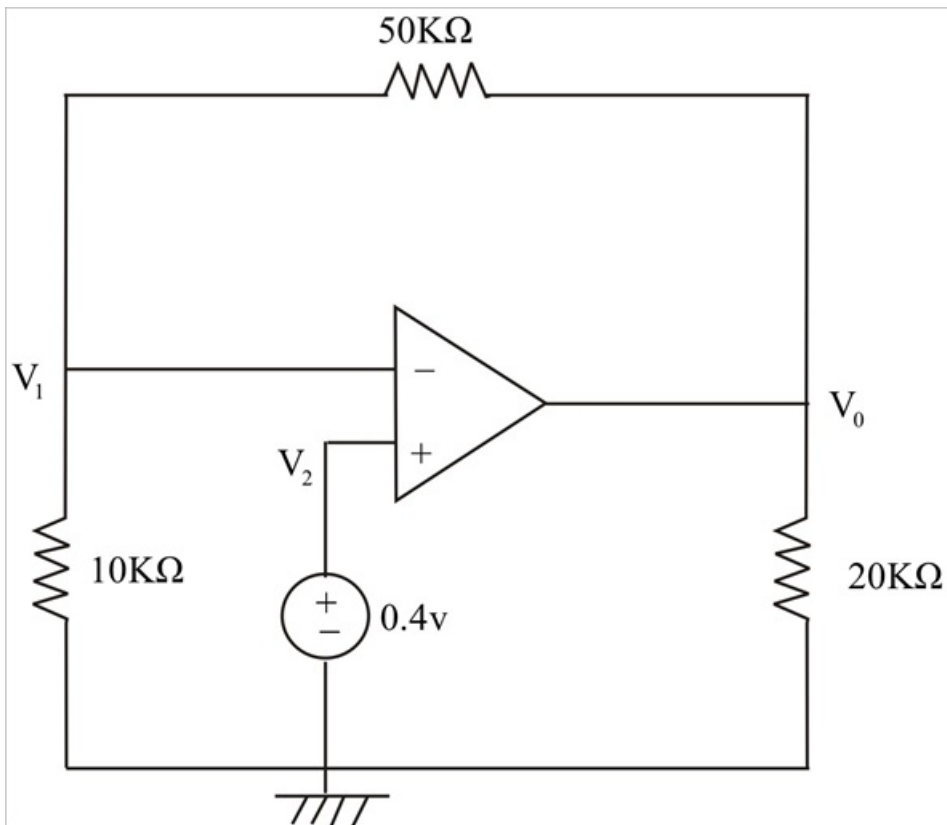


Fig-1

Step 2 of 4

From Fig-1,

At node 1,

$$\frac{0 - V_1}{10 \times 10^3} = \frac{V_1 - V_0}{50 \times 10^3} \dots \dots \dots (1)$$

But,

$$V_1 = 0.4V$$

From Equation-(1),

$$-5V_1 = V_1 - V_0$$

$$V_0 = 6V_1$$

$$V_0 = 6 \times 0.4$$

$$V_0 = 2.4V$$

Step 3 of 4

Alternatively, viewed as a non-inverting amplifier,

For non-inverting amplifier gain is,

$$V_0 = \left(1 + \frac{R_f}{R_i}\right) V_i$$

$$V_0 = \left(1 + \left(\frac{50}{10}\right)\right) \times 0.4$$

Therefore,

$$V_0 = 2.4V$$

Step 4 of 4

Therefore,

$$i_0 = \frac{V_0}{R_{20k\Omega}}$$

$$i_0 = \frac{2.4}{20 \times 10^3}$$

$$\boxed{i_0 = 0.12mA}$$