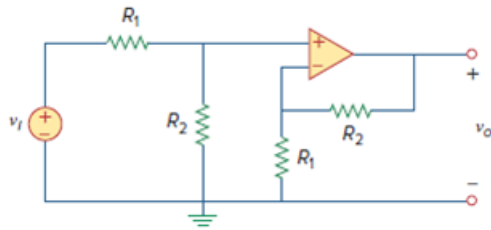


## Problem

Determine the voltage gain  $v_o/v_i$  of the op amp circuit in Fig. 5.67.

**Figure. 5.67:**




## Step-by-step solution

## Step 1 of 3

Refer to Figure 5.67 in the textbook.

The modified circuit is shown in Figure 1.

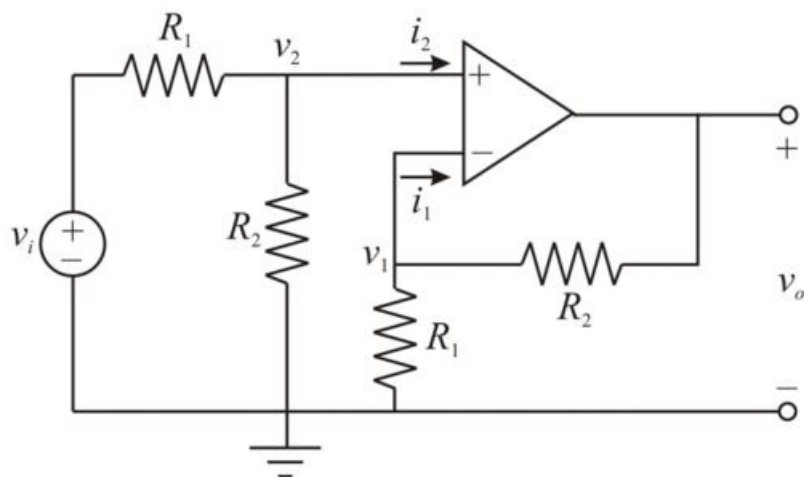

**Figure 1**

## Step 2 of 3

In an ideal op-amp, the inverting and non-inverting terminal currents are zero because of infinite input impedance, thus,

$$i_1 = 0 \text{ A}$$

$$i_2 = 0 \text{ A}$$

The inverting and non-inverting node voltages are equal due to virtual short circuit, thus,

$$v_1 = v_2 \dots\dots (1)$$

Applying Kirchhoff's current law at node  $v_2$ .

$$\frac{v_2 - v_i}{R_1} + \frac{v_2}{R_2} = 0$$

$$v_2 \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{v_i}{R_1} = 0$$

$$v_2 \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{v_i}{R_1}$$

$$v_2 \left[ \frac{R_1 + R_2}{R_1 R_2} \right] = \frac{v_i}{R_1}$$

$$v_2 \left[ \frac{R_1 + R_2}{R_2} \right] = v_i$$

$$v_2 = v_i \left[ \frac{R_2}{R_1 + R_2} \right]$$

Since  $v_1 = v_2$ , therefore, substitute  $v_i \left[ \frac{R_2}{R_1 + R_2} \right]$  for  $v_2$  in equation (1).

$$v_1 = v_i \left[ \frac{R_2}{R_1 + R_2} \right] \dots\dots (2)$$

### Step 3 of 3

Applying Kirchhoff's current law at node  $v_1$ .

$$\frac{v_1}{R_1} + \frac{v_1 - v_o}{R_2} = 0$$

$$v_1 \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{v_o}{R_2} = 0$$

$$v_1 \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{v_o}{R_2}$$

$$v_1 \left[ \frac{R_1 + R_2}{R_1 R_2} \right] = \frac{v_o}{R_2}$$

$$v_o = v_1 \left[ \frac{R_1 + R_2}{R_1} \right] \dots\dots (3)$$

Substitute  $v_i \left[ \frac{R_2}{R_1 + R_2} \right]$  for  $v_1$  in equation (3).

$$v_o = v_i \left[ \frac{R_2}{R_1 + R_2} \right] \left[ \frac{R_1 + R_2}{R_1} \right]$$

$$v_o = v_i \left[ \frac{R_2}{R_1} \right]$$

$$\frac{v_o}{v_i} = \frac{R_2}{R_1}$$

Hence, the voltage gain  $\frac{v_o}{v_i}$  is  $\boxed{\frac{R_2}{R_1}}$ .