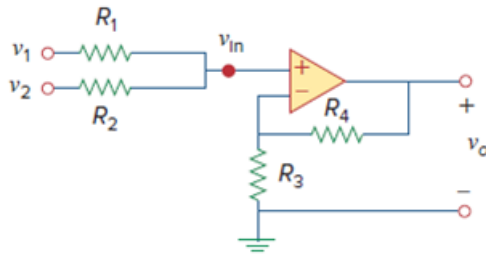


Problem

Given the op amp circuit shown in Fig. 5.72, express v_o in terms of v_1 and v_2 .

Figure. 5.72:



Step-by-step solution

Step 1 of 2

Refer to Figure 5.72 in the textbook.

Apply Kirchhoff's Current Law.

$$\frac{v_1 - v_{in}}{R_1} + \frac{v_2 - v_{in}}{R_2} = 0 \quad \dots\dots (1)$$

Consider the voltage at the inverting terminal is v_a .

Use the voltage divider rule.

$$v_a = \frac{R_3}{R_3 + R_4} v_o \quad \dots\dots (2)$$

Since,

$$v_a = v_{in} \quad (\text{By the concept of virtual ground}).$$

Step 2 of 2

Combining equations (1) and (2), we get,

$$\frac{v_1 - \frac{R_3}{R_3 + R_4} v_0}{R_1} + \frac{v_2 - \frac{R_3}{R_3 + R_4} v_0}{R_2} = 0$$

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} - \left(\frac{R_3}{R_3 + R_4} v_0 \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = 0$$

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} = \left(\frac{R_3}{R_3 + R_4} v_0 \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$v_1 R_2 + v_2 R_1 = \frac{R_3 (R_1 + R_2)}{R_3 + R_4} v_0$$

$$v_0 = \frac{R_3 + R_4}{R_3 (R_1 + R_2)} (v_1 R_2 + v_2 R_1)$$

$$v_0 = \frac{R_3 + R_4}{R_3 \left(1 + \frac{R_1}{R_2} \right)} \left(v_1 + \frac{R_1}{R_2} v_2 \right)$$

Therefore, the voltage, v_0 is $\boxed{\frac{R_3 + R_4}{R_3 \left(1 + \frac{R_1}{R_2} \right)} \left(v_1 + \frac{R_1}{R_2} v_2 \right)}$.