

Problem

The feedback resistor of a three-input averaging summing amplifier is 50 kΩ. What are the values of R_1 , R_2 , and R_3 ?

Step-by-step solution

Step 1 of 4

The output equation of three input summing amplifier is,

$$v_0 = -R_f \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right)$$

$$v_0 = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right) \dots\dots (1)$$

An averaging amplifier is a summer that provides an output equal to the average of the inputs. The output equation of averaging amplifier with three inputs is,

$$v_0 = -\frac{1}{3}(v_1 + v_2 + v_3)$$

$$v_0 = - \left(\frac{1}{3} v_1 + \frac{1}{3} v_2 + \frac{1}{3} v_3 \right) \dots\dots (2)$$

Step 2 of 4

Compare first terms of equations (1) and (2) to get the value of R_1 .

$$\frac{R_f}{R_1} = \frac{1}{3}$$

$$R_1 = 3 R_f$$

Substitute 50 kΩ for R_f .

$$R_1 = 3(50 \times 10^3)$$

$$R_1 = 150 \text{ k}\Omega$$

Therefore, the value of R_1 , is 150 kΩ.

Step 3 of 4

Compare second terms of equations (1) and (2) to get the value of R_2 .

$$\frac{R_f}{R_2} = \frac{1}{3}$$

$$R_2 = 3 R_f$$

Substitute 50 kΩ for R_f .

$$R_2 = 3(50 \times 10^3)$$

$$R_2 = 150 \text{ k}\Omega$$

Therefore, the value of R_2 , is 150 kΩ.

Compare third terms of equations (1) and (2) to get the value of R_3 .

$$\frac{R_f}{R_3} = \frac{1}{3}$$

$$R_3 = 3 R_f$$

Substitute $50\text{ k}\Omega$ for R_f .

$$R_3 = 3(50 \times 10^3)$$

$$R_3 = 150\text{ k}\Omega$$

Therefore, the value of R_3 , is $150\text{ k}\Omega$.