

Problem

Design a difference amplifier to have a gain of 4 and a common-mode input resistance of $20\text{ k}\Omega$ at each input.

Step-by-step solution

Step 1 of 6

Draw the difference amplifier circuit diagram as shown in Figure 1.

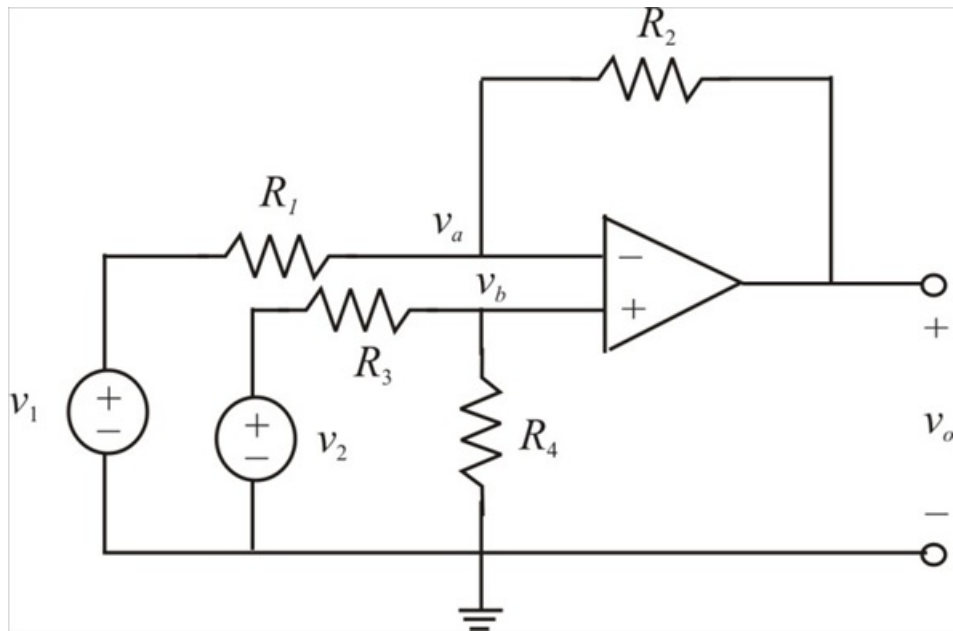


Figure 1

Step 2 of 6

The circuit is labeled as shown in Figure 2.

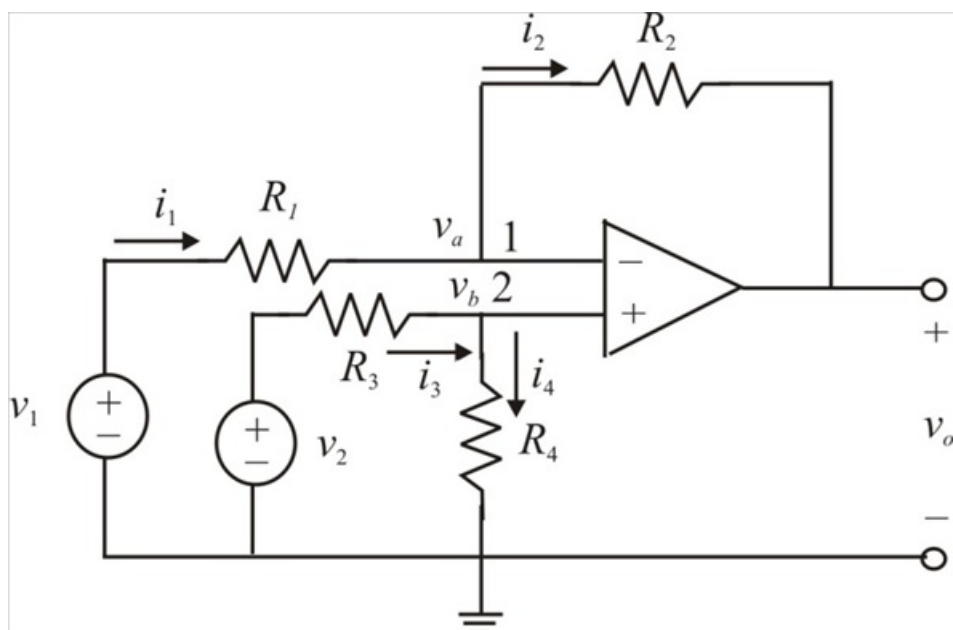


Figure 2

Step 3 of 6

The gain of the difference amplifier = 4

The common-mode input resistance = $20\text{ k}\Omega$

The currents i_1 and i_2 entering in to the op amp is zero for an ideal amplifier.

Applying Kirchhoff's current law to node 1,

$$i_1 = i_2$$

$$\frac{v_1 - v_a}{R_1} = \frac{v_a - v_o}{R_2}$$

$$v_o = \left(\frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1$$

$$\text{Therefore } v_o = \left(\frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1 \dots\dots (1)$$

Applying Kirchhoff's current law to node 2,

$$i_3 = i_4$$

$$\frac{v_2 - v_b}{R_3} = \frac{v_b - 0}{R_4}$$

$$v_b = \frac{R_4}{R_3 + R_4} v_2$$

$$\text{Therefore } v_b = \frac{R_4}{R_3 + R_4} v_2 \dots\dots (2)$$

Step 4 of 6

But $v_a = v_b$ for an ideal op amp, substituting the equation (2) in equation (1), we get

$$\begin{aligned} v_o &= \left(\frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1 \\ &= \frac{R_2 (1 + R_1 / R_2)}{R_1 (1 + R_3 / R_4)} v_2 - \frac{R_2}{R_1} v_1 \end{aligned}$$

Since a difference amplifier must reject a signal common to the two inputs, the amplifier must have the property that $v_o = 0$ when $v_1 = v_2$.

This property exist when

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Step 5 of 6

When the op amp circuit is a difference amplifier v_o becomes,

$$v_o = \frac{R_2}{R_1}(v_2 - v_1)$$

Hence the gain is

$$\frac{v_o}{v_2 - v_1} = \frac{R_2}{R_1} = 4$$

$$R_2 = 4 R_1$$

But

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} = \frac{1}{4}$$

$$R_4 = 4 R_3$$

If $R_1 = 20 \text{ k}\Omega$, then the resistance R_2 is:

$$R_2 = 4 R_1$$

$$= 4(20 \times 10^3)$$

$$= 80 \text{ k}\Omega$$

Therefore the resistance R_2 is $80 \text{ k}\Omega$.

If $R_3 = 20 \text{ k}\Omega$, then the resistance R_4 is:

$$R_4 = 4 R_3$$

$$= 4(20 \times 10^3)$$

$$= 80 \text{ k}\Omega$$

Therefore the resistance R_4 is $80 \text{ k}\Omega$.

Step 6 of 6

The desired difference amplifier circuit diagram as shown in Figure 3.

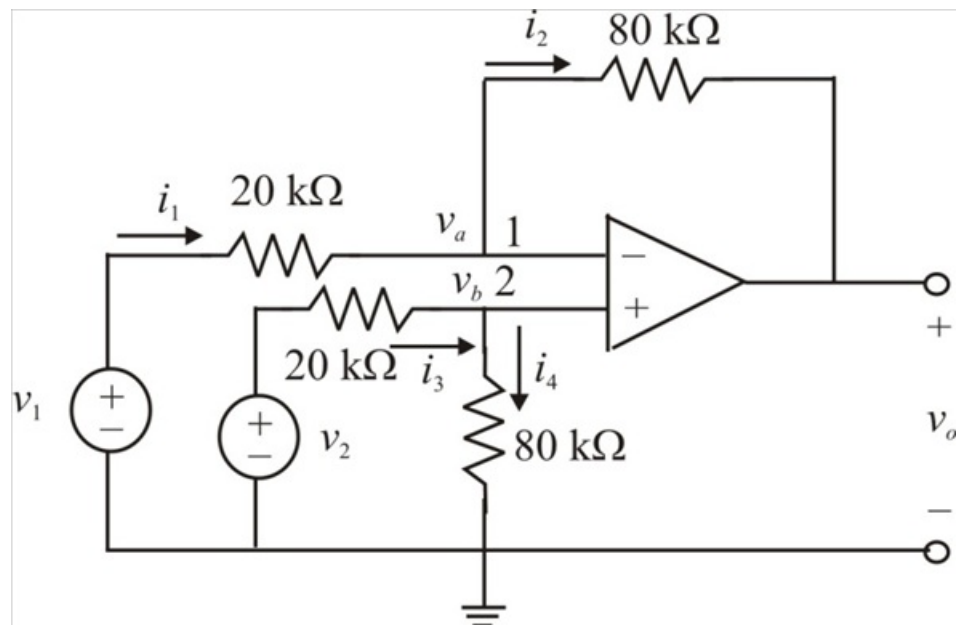


Figure 3