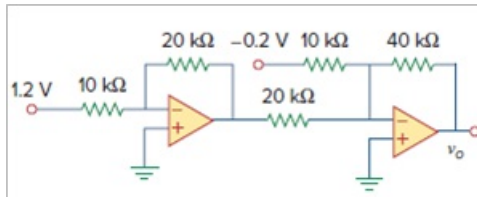


Problem

Determine v_o in the circuit of Fig. 5.88.

Figure 5.88:



Step-by-step solution

Step 1 of 3

Refer to Figure 5.88 in the textbook and assign nodes, the modified circuit is shown in Figure 1.

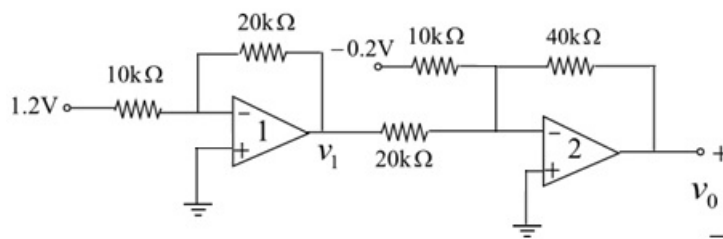


Figure 1

Step 2 of 3

In Figure 1, the first op-amp circuit is act as an inverting amplifier circuit. The output voltage is,

$$\begin{aligned}
 v_1 &= -\left(\frac{R_f}{R_i}\right)v_i \\
 &= -\left(\frac{20 \times 10^3}{10 \times 10^3}\right)(1.2) \\
 &= -2(1.2) \\
 v_1 &= -2.4 \text{ V}
 \end{aligned}$$

Step 3 of 3

In Figure 1, the second op-amp circuit is act as a two input summing amplifier circuit. The output voltage is,

$$\begin{aligned}v_0 &= -R_f \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} \right) \\&= -40 \times 10^3 \left(\frac{-0.2}{10 \times 10^3} + \frac{v_1}{20 \times 10^3} \right) \\&= 0.8 - 2v_1\end{aligned}$$

Substitute -2.4 V for v_1 .

$$\begin{aligned}v_0 &= 0.8 - 2(-2.4) \\&= 0.8 + 4.8 \\v_0 &= 5.6 \text{ V}\end{aligned}$$

Therefore, the output voltage, v_0 is 5.6 V.