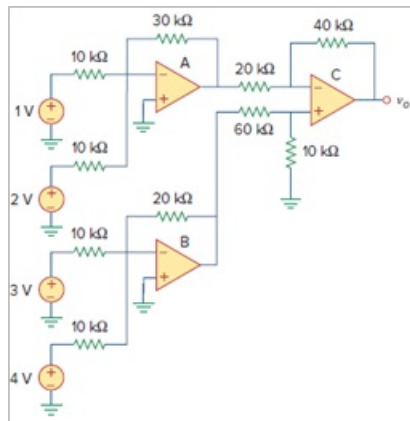


Problem

Determine v_o in the op amp circuit of Fig. 5.96.

Figure 5.96:



Step-by-step solution

Step 1 of 5

Refer to circuit diagram in Figure 5.96 in the textbook.

Draw the modified circuit as shown in Figure 1.

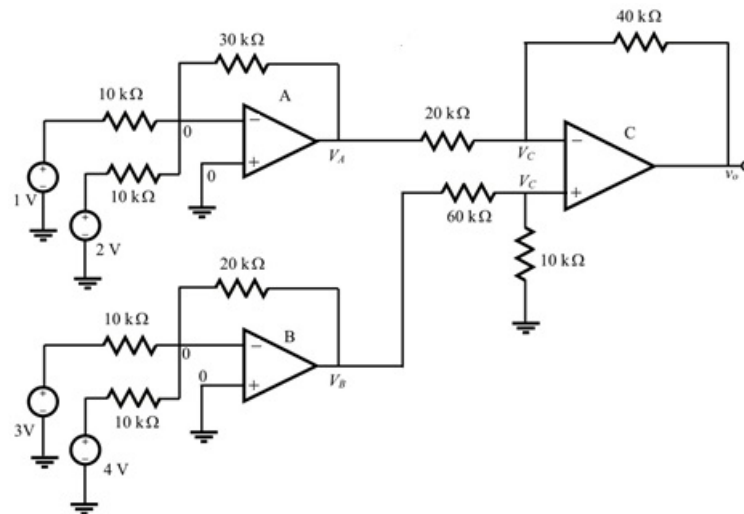


Figure 1

Step 2 of 5

Apply Kirchhoff's current law at node 0 of op-amp A.

Determine the voltage at V_A .

$$\begin{aligned}\frac{0-1}{10 \times 10^3} + \frac{0-2}{10 \times 10^3} + \frac{0-V_A}{30 \times 10^3} &= 0 \\ \frac{V_A}{30 \times 10^3} &= \frac{-1}{10 \times 10^3} + \frac{-2}{10 \times 10^3} \\ V_A &= \left(\frac{-3}{10 \times 10^3} \right) (30 \times 10^3) \\ V_A &= -9 \text{ V}\end{aligned}$$

Step 3 of 5

Apply Kirchhoff's current law at node 0 of op-amp B.

Determine the voltage at V_B .

$$\begin{aligned}\frac{0-3}{10 \times 10^3} + \frac{0-4}{10 \times 10^3} + \frac{0-V_B}{20 \times 10^3} &= 0 \\ \frac{-3}{10 \times 10^3} + \frac{-4}{10 \times 10^3} &= \frac{V_B}{20 \times 10^3} \\ V_B &= \left(\frac{-7}{10 \times 10^3} \right) (20 \times 10^3) \\ V_B &= -14 \text{ V}\end{aligned}$$

Step 4 of 5

Apply Kirchhoff's current law at non-inverting terminal of op-amp C.

Determine the voltage at V_C .

$$\begin{aligned}\frac{V_C}{10 \times 10^3} + \frac{V_C - V_B}{60 \times 10^3} &= 0 \\ \left(\frac{1}{10 \times 10^3} + \frac{1}{60 \times 10^3} \right) V_C &= \frac{V_B}{60 \times 10^3} \\ \text{Substitute } -14 \text{ V for } V_B. \\ \left(\frac{6+1}{60 \times 10^3} \right) V_C &= -\frac{14}{60 \times 10^3} \\ V_C &= \left(-\frac{14 \text{ V}}{60 \times 10^3} \right) \left(\frac{60 \times 10^3}{7} \right) \\ &= -2 \text{ V}\end{aligned}$$

Step 5 of 5

Determine the voltage at v_o .

Apply Kirchhoff's current law at inverting terminal of op-amp C.

$$\frac{V_C - V_A}{20 \times 10^3} + \frac{V_C - v_o}{40 \times 10^3} = 0$$

$$V_C \left(\frac{1}{20 \times 10^3} + \frac{1}{40 \times 10^3} \right) - \frac{V_A}{20 \times 10^3} - \frac{v_o}{40 \times 10^3} = 0$$

$$3V_C - 2V_A - v_o = 0$$

$$v_o = 3V_C - 2V_A$$

Substitute -2 V for V_C , and -9 V for V_A in equation.

$$\begin{aligned} v_o &= 3(-2) - (2)(-9) \\ &= 12 \text{ V} \end{aligned}$$

Therefore, the output voltage v_o is $\boxed{12 \text{ V}}$.