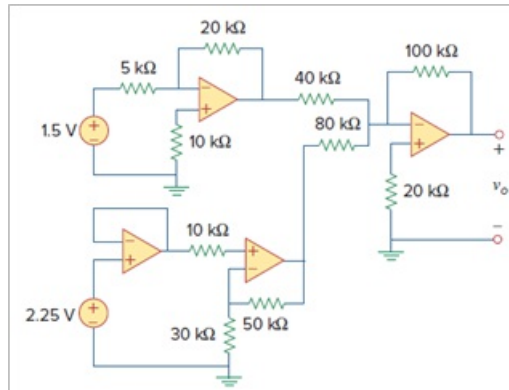


Problem

Determine v_o in the op amp circuit of Fig. 5.97.

Figure 5.97:



Step-by-step solution

Step 1 of 5

Draw the circuit diagram as shown in Figure 1.

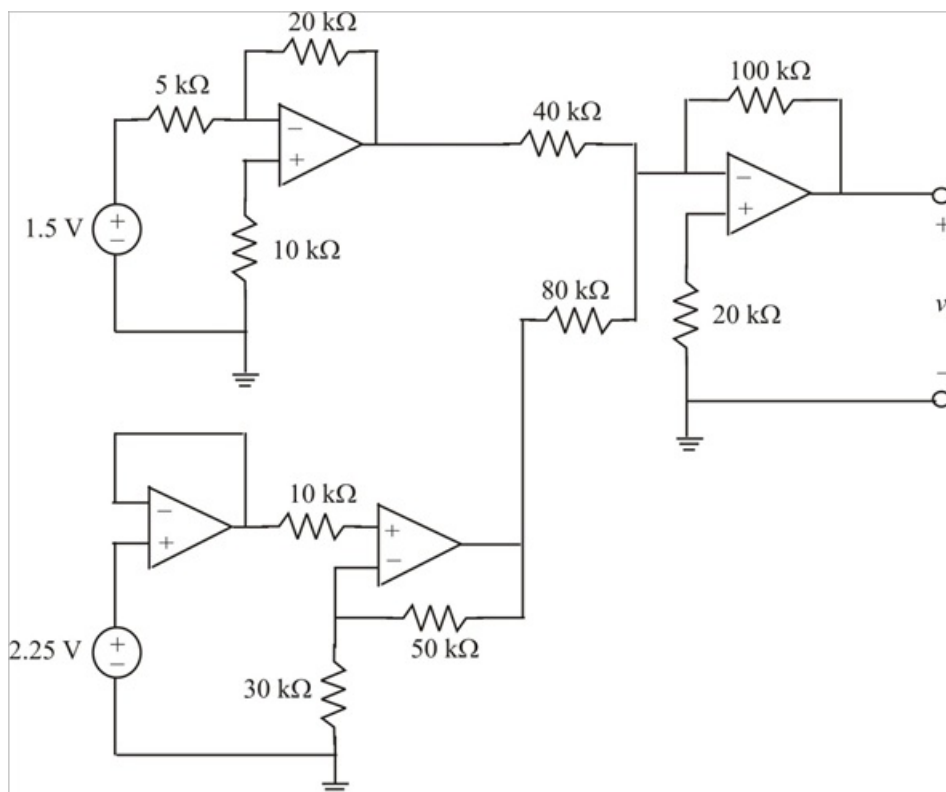


Figure 1

Step 2 of 5

The circuit is labeled as shown in Figure 2.

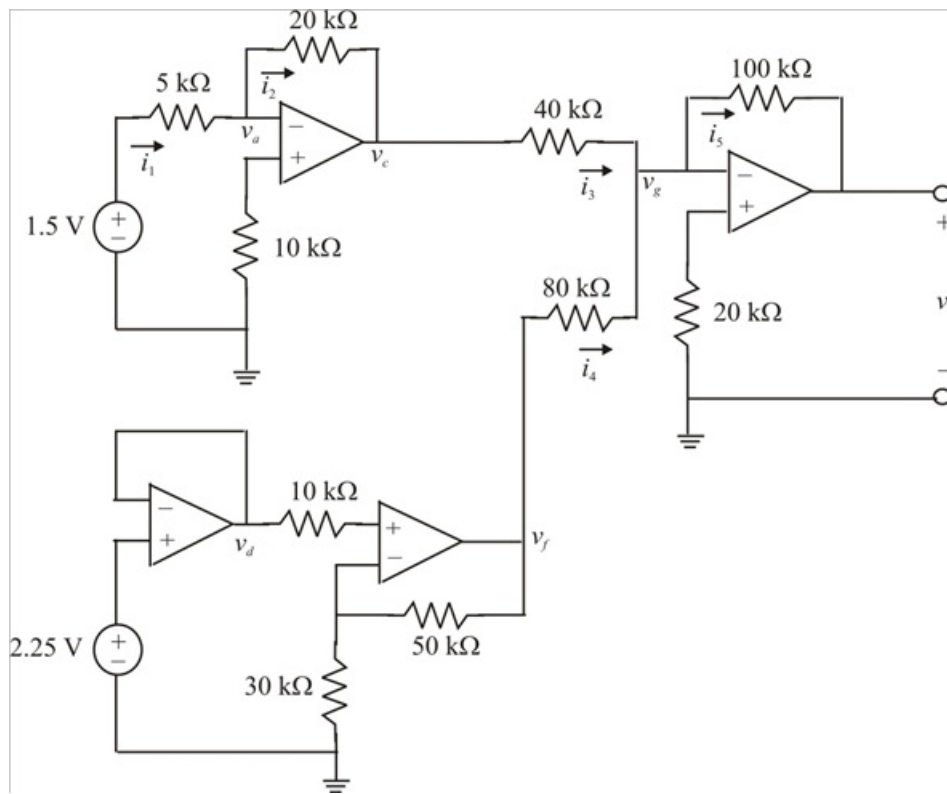


Figure 2

Step 3 of 5

Applying Kirchhoff's current law to node v_a ,

$$i_1 = i_2$$

$$\frac{1.5 - v_a}{5} = \frac{v_a - v_c}{20}$$

$$6 - 4v_a = v_a - v_c$$

$$5v_a - v_c = 6$$

Therefore $5v_a - v_c = 6$ (1)

But $v_a = 0$ since non-inverting terminal is grounded. Then equation (1) becomes,

$$5v_a - v_c = 6$$

$$5(0) - v_c = 6$$

$$v_c = -6 \text{ V}$$

Therefore $v_c = -6 \text{ V}$ (2)

Step 4 of 5

For the voltage follower, the voltage v_d is:

$$v_d = 2.25 \text{ V}$$

Therefore $v_d = 2.25 \text{ V}$ (3)

The output voltage v_f of a non-inverting amplifier is:

$$v_f = \left(1 + \frac{R_f}{R_i} \right) v_i$$

Where

$$R_f = 50 \text{ k}\Omega$$

$$R_i = 30 \text{ k}\Omega$$

$$v_i = v_d = 2.25 \text{ V}$$

The voltage v_f is:

$$\begin{aligned} v_f &= \left(1 + \frac{50}{30} \right) (2.25) \\ &= 6 \text{ V} \end{aligned}$$

Therefore $v_f = 6 \text{ V}$ (4)

Applying Kirchhoff's current law to node v_g ,

$$i_3 + i_4 = i_5$$

$$\frac{v_c - v_g}{40} + \frac{v_f - v_g}{80} = \frac{v_g - v_o}{100}$$

$$10v_c - 10v_g + 5v_f - 5v_g = 4v_g - 4v_o$$

$$10v_c - 19v_g + 5v_f = -4v_o$$

Therefore $10v_c - 19v_g + 5v_f = -4v_o$ (5)

Step 5 of 5

But $v_g = 0$ since non-inverting terminal is grounded. Then equation (5) becomes,

$$10v_c - 19v_g + 5v_f = -4v_o$$

$$10v_c - 19(0) + 5v_f = -4v_o$$

$$10v_c + 5v_f = -4v_o$$

Therefore $10v_c + 5v_f = -4v_o$ (6)

Substituting equation (2) and (4) in equation (6), we get

$$10v_c + 5v_f = -4v_o$$

$$10(-6) + 5(6) = -4v_o$$

$$-60 + 30 = -4v_o$$

$$v_o = 7.5 \text{ V}$$

Therefore the output voltage v_o is 7.5 V.