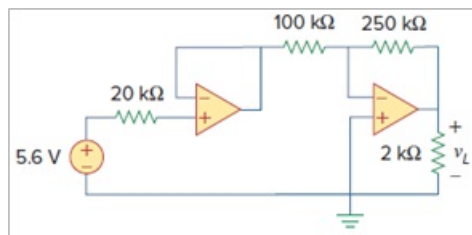


Problem

Find the load voltage v_L in the circuit of Fig. 5.98.

Figure. 5.98:



Step-by-step solution

Step 1 of 2

Draw the circuit diagram as shown in Figure 1.

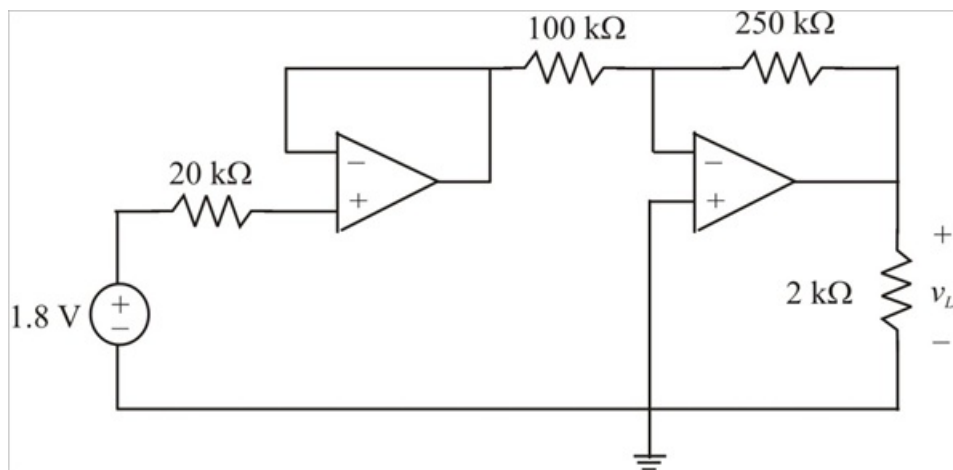


Figure 1

Step 2 of 2

Since no current flows into the input terminals of the ideal op amp, there is no current flow through the 20 k Ω resistor.

Hence the output voltage of the voltage follower (output of first op amp) is 1.8 V

The second amplifier is an inverting amplifier, the output voltage of an inverting amplifier is given by:

$$v_o = -\frac{R_f}{R_i} v_i$$

Where

$$R_f = 250 \text{ k}\Omega$$

$$R_i = 100 \text{ k}\Omega$$

$$v_i = 1.8 \text{ V}$$

The output voltage v_L of the amplifier is calculated as:

$$\begin{aligned} v_L &= -\frac{250}{100}(1.8) \\ &= -(2.5)(1.8) \\ &= -4.5 \text{ V} \end{aligned}$$

Therefore the output voltage v_L is -4.5 V.