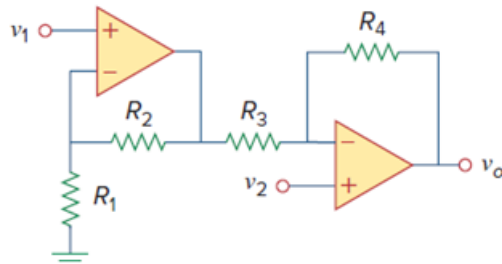


Problem

Figure 5.105 displays a two-op-amp instrumentation amplifier. Derive an expression for v_o in terms of v_1 and v_2 . How can this amplifier be used as a subtractor?

Figure 5.105:




Step-by-step solution

Step 1 of 4

Refer to Figure 5.105 in the text book for the two op-amp instrumentation amplifier circuit.

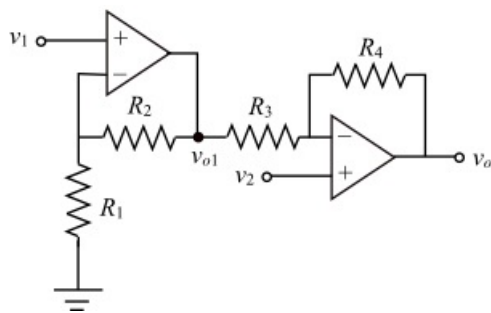Redraw the circuit by marking the output voltage of the first op-amp.



According to virtual ground concept, the voltage at the inverting input of the first op-amp is equal to v_1 , and the voltage at the inverting terminal of the second op-amp is equal to v_2 .

Step 2 of 4

Apply Kirchhoff's current law at the inverting terminal of the first op-amp.

$$\frac{v_1}{R_1} + \frac{v_1 - v_{o1}}{R_2} = 0$$

$$\frac{v_{o1}}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) v_1$$

$$v_{o1} = R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) v_1$$

$$= \left(1 + \frac{R_2}{R_1} \right) v_1$$

Step 3 of 4

Apply Kirchhoff's current law at the inverting terminal of the second op-amp.

$$\frac{v_2 - v_{o1}}{R_3} + \frac{v_2 - v_o}{R_4} = 0$$

$$\left(\frac{1}{R_3} + \frac{1}{R_4} \right) v_2 - \frac{v_{o1}}{R_3} = \frac{v_o}{R_4}$$

Substitute $\left(1 + \frac{R_2}{R_1} \right) v_1$ for v_{o1} .

$$\left(\frac{1}{R_3} + \frac{1}{R_4} \right) v_2 - \frac{1}{R_3} \left(1 + \frac{R_2}{R_1} \right) v_1 = \frac{v_o}{R_4}$$

$$v_o = R_4 \left[\left(\frac{1}{R_3} + \frac{1}{R_4} \right) v_2 - \frac{1}{R_3} \left(1 + \frac{R_2}{R_1} \right) v_1 \right]$$

$$= \left(1 + \frac{R_4}{R_3} \right) v_2 - \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1} \right) v_1$$

$$= \left(1 + \frac{R_4}{R_3} \right) v_2 - \left(\frac{R_4}{R_3} + \frac{R_2 R_4}{R_1 R_3} \right) v_1$$

Thus, the expression for v_o is $\boxed{\left(1 + \frac{R_4}{R_3} \right) v_2 - \left(\frac{R_4}{R_3} + \frac{R_2 R_4}{R_1 R_3} \right) v_1}$.

Step 4 of 4

To use the amplifier as a subtractor, the gains of the two inputs should be equal.

$$1 + \frac{R_4}{R_3} = \frac{R_4}{R_3} + \frac{R_2 R_4}{R_1 R_3}$$

$$\frac{R_2 R_4}{R_1 R_3} = 1$$

$$R_2 R_4 = R_1 R_3$$

$$\frac{R_1}{R_2} = \frac{R_4}{R_3}$$

Write the expression for the output voltage.

$$v_o = \left(1 + \frac{R_4}{R_3} \right) v_2 - \left(\frac{R_4}{R_3} + \frac{R_2 R_4}{R_1 R_3} \right) v_1$$

$$= \left(1 + \frac{R_4}{R_3} \right) v_2 - \left(\frac{R_4}{R_3} + 1 \right) v_1$$

$$= \left(1 + \frac{R_4}{R_3} \right) (v_2 - v_1)$$

(or)

$$v_o = \left(1 + \frac{R_1}{R_2} \right) (v_2 - v_1)$$

Thus, the amplifier can be used as a subtractor by making the ratios of the resistors equal, that

is, $\boxed{\frac{R_1}{R_2} = \frac{R_4}{R_3}}$ or by making $\boxed{R_1 = R_4}$ and $\boxed{R_2 = R_3}$.

The subtractor has a gain of $\left(1 + \frac{R_4}{R_3} \right)$, which is equal to $\left(1 + \frac{R_1}{R_2} \right)$.