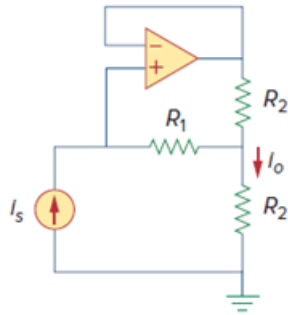


Problem


A noninverting current amplifier is portrayed in Fig. 5.108. Calculate the gain i_o/i_s . Take $R_1 = 8 \text{ k}\Omega$ and $R_2 = 1 \text{ k}\Omega$.

Figure 5.108:



Step-by-step solution

Step 1 of 2

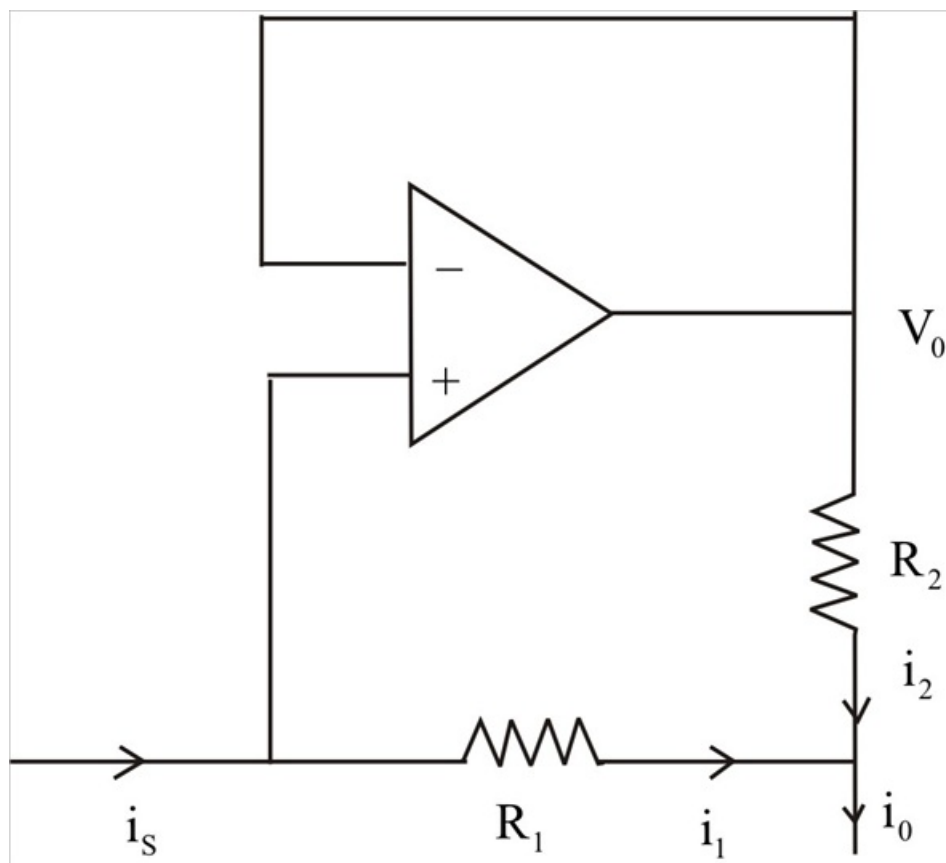

Step 2 of 2

$$i_0 = i_1 + i_2 \rightarrow (1)$$

But $i_1 = i_s \rightarrow (2)$

R1 and R2 have the same voltage, V0, across them,

$$R_1 i_1 = R_2 i_2, \text{ which leads to } i_2 = \left(\frac{R_1}{R_2} \right) i_1 \rightarrow (3)$$

Substituting (2) and (3) into (1) gives,

$$i_0 = i_s \left(1 + \frac{R_1}{R_2} \right) .$$

$$\frac{i_0}{i_s} = \left(1 + \frac{R_1}{R_2} \right) = 1 + \frac{8}{1} = 9 .$$