

Problem

If the voltage across a 7.5-F capacitor is $2te^{-3t}$ V, find the current and the power.

Step-by-step solution

Step 1 of 1

The value of capacitance, $C = 7.5$ F

The voltage across capacitor, $v(t) = 2te^{-3t}$ V

Determine the current through the capacitor.

$$\begin{aligned} i(t) &= C \frac{dv(t)}{dt} \\ &= (7.5) \frac{d}{dt} (2te^{-3t}) \\ &= (7.5 \times 2) [e^{-3t} + t(-3)e^{-3t}] \\ &= 15 [e^{-3t} (1 - 3t)] \text{ A} \end{aligned}$$

Thus, the current through the capacitor is $15[(1 - 3t)e^{-3t}]$ A .

Determine the power in the capacitor using the following formula:

$$\begin{aligned} p(t) &= v(t) \times i(t) \\ p(t) &= 15 [e^{-3t} (1 - 3t)] (2te^{-3t}) \\ &= 30t (1 - 3t) e^{-6t} \text{ W} \end{aligned}$$

Thus, the power in the capacitor is $30t(1 - 3t)e^{-6t}$ W .