

Chapter 6, Problem 3PP

Problem

The current through a $100\text{-}\mu\text{F}$ capacitor is $i(t) = 50 \sin 120\pi t$ mA. Calculate the voltage across it at $t = 1$ ms and $t = 5$ ms. Take $v(0) = 0$.

Step-by-step solution

Step 1 of 3

Refer to equation 6.6 in the textbook.

The voltage across the capacitor is,

$$v = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$

Here, $v(t_0)$ is the voltage across the capacitor at time t_0 sec.

Substitute 0 for t_0 .

$$v = \frac{1}{C} \int_0^t i dt + v(0)$$

Substitute 0 for $v(0)$, 100×10^{-6} for C, and $50 \times 10^{-3} \sin(120\pi t)$ for i .

$$\begin{aligned} v &= \frac{1}{100 \times 10^{-6}} \int_0^t 50 \times 10^{-3} \sin(120\pi t) dt + 0 \\ &= \frac{50 \times 10^{-3}}{100 \times 10^{-6}} \int_0^t \sin(120\pi t) dt \\ &= 500 \left[\frac{-\cos(120\pi t)}{120\pi} \right]_0^t \\ &= \frac{500}{120\pi} \times [-\cos 120\pi(t) - (-\cos 120\pi(0))] \end{aligned}$$

Therefore,

$$v = 1.3263 \times [-\cos 120\pi t + 1] \dots\dots (1)$$

Step 2 of 3

Recall equation (1).

$$v = 1.3263 \times [-\cos 120\pi t + 1]$$

Substitute 10^{-3} for t .

$$\begin{aligned} v &= 1.3263 [-\cos 120\pi \times 10^{-3} + 1] \\ &= 1.3263(0.0702235) \\ &= 93.14 \text{ mV} \end{aligned}$$

Therefore, the voltage across the capacitor at $t = 1$ ms is **93.14 mV**.

Step 3 of 3

Recall equation (1).

$$v = 1.3263 \times [-\cos 120\pi t + 1]$$

Substitute 5×10^{-3} for t .

$$\begin{aligned} v &= 1.3263 [-\cos 120\pi \times 5 \times 10^{-3} + 1] \\ &= 1.3263(1.309016994) \\ &= 1.736 \text{ V} \end{aligned}$$

Therefore, the voltage across the capacitor at $t = 5 \text{ ms}$ is 1.736 V.