

Problem

A voltage across a capacitor is equal to $[2 - 2 \cos(4t)]$ V and the current flowing through it is equal to $2 \sin(4t)$ μ A. Determine the value of the capacitance. Calculate the power being stored by the capacitor.

Step-by-step solution

Step 1 of 2

The capacitor current is,

$$i(t) = C \frac{dv(t)}{dt}$$

Substitute $2 - 2 \cos(4t)$ V for $v(t)$ and $2 \sin(4t)$ μ A for $i(t)$.

$$2 \sin(4t) \times 10^{-6} = C \frac{d}{dt} [2 - 2 \cos(4t)]$$

$$2 \times 10^{-6} \sin(4t) = C(-2)(-4 \sin 4t)$$

$$\frac{2 \times 10^{-6} \sin(4t)}{8 \sin 4t} = C$$

$$\frac{10^{-6}}{4} = C$$

$$C = 0.25 \times 10^{-6}$$

$$= 0.25 \mu\text{F}$$

Thus, the value of the capacitor is $0.25 \mu\text{F}$.

Step 2 of 2

The expression for the power is,

$$p(t) = v(t)i(t)$$

Substitute $2 - 2 \cos(4t)$ V for $v(t)$ and $2 \sin(4t)$ μ A for $i(t)$.

$$p(t) = (2 - 2 \cos(4t))(2 \sin(4t) \times 10^{-6})$$

$$= 4(1 - \cos(4t)) \sin(4t) \mu\text{W}$$

Thus, the power being stored in the capacitor is $4(1 - \cos(4t)) \sin(4t) \mu\text{W}$.