


Problem

Can the voltage waveform in Fig. 6.42 be associated with a real capacitor?

(a) Yes

(b) No

Fig. 6.42:

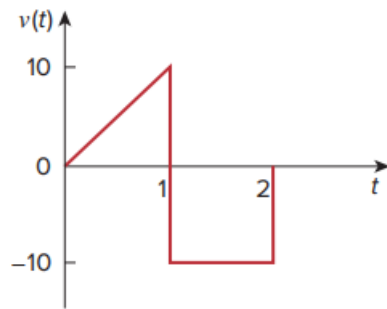

Step-by-step solution

Step 1 of 1

6.4

(b)