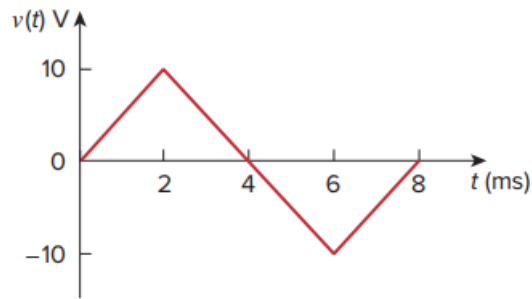


Problem

The voltage across a $4\text{-}\mu\text{F}$ capacitor is shown in Fig. 6.45. Find the current waveform.

Fig. 6.45:



Step-by-step solution

Step 1 of 7

Refer to Figure 6.45 in the textbook.

Consider the formula for straight line equation for two points (x_1, y_1) and (x_2, y_2) .

$$(y - y_1) = \frac{y_2 - y_1}{x_2 - x_1} (x - x_1)$$

Where,

$$y = v(t)$$

$$x = t$$

Step 2 of 7

For $0 \leq t < 2$ ms, calculate the straight line equation of points $(0, 0)$ and $(2\text{m}, 10)$.

$$(y - 0) = \frac{10 - 0}{2 \times 10^{-3} - 0} (x - 0)$$

$$y = \frac{10}{2 \times 10^{-3}} x$$

$$y = 5000x$$

$$v(t) = 5000t \quad \text{for } 0 \leq t < 2 \text{ ms}$$

Step 3 of 7

For $2 \text{ ms} \leq t < 6 \text{ ms}$, calculate the straight line equation of points $(2\text{ms}, 10)$ and $(6\text{ms}, -10)$

$$(y - 10) = \frac{-10 - 10}{6 \times 10^{-3} - 2 \times 10^{-3}} (x - 2 \times 10^{-3})$$

$$(y - 10) = \frac{-20}{4 \times 10^{-3}} (x - 2 \times 10^{-3})$$

$$y - 10 = -5000x + 10$$

$$y = -5000x + 20$$

$$v(t) = -5000t + 20 \quad \text{for } 2 \text{ ms} \leq t < 6 \text{ ms}$$

Step 4 of 7

For $6 \text{ ms} \leq t < 8 \text{ ms}$, calculate the straight line equation of points $(6\text{ms}, -10)$ and $(8\text{ms}, 0)$.

$$(y - (-10)) = \frac{0 + 10}{8 \times 10^{-3} - 6 \times 10^{-3}} (x - 6 \times 10^{-3})$$

$$y + 10 = 5000(x - 6 \times 10^{-3})$$

$$y + 10 = 5000x - 30$$

$$y = 5000x - 40$$

$$v(t) = 5000t - 40 \quad \text{for } 6 \text{ ms} \leq t < 8 \text{ ms}$$

Step 5 of 7

Therefore, the voltage values are,

$$v(t) = \begin{cases} 5000t & 0 < t < 2 \text{ ms} \\ 20 - 5000t & 2 \text{ ms} < t < 6 \text{ ms} \\ -40 + 5000t & 6 \text{ ms} < t < 8 \text{ ms} \end{cases}$$

Write the expression for the current through the capacitor.

$$i(t) = C \frac{dv}{dt}$$

Calculate the current through the current through the capacitor for $0 < t < 2 \text{ ms}$.

$$\begin{aligned} i(t) &= (4 \times 10^{-6}) \frac{d}{dt} (5000t) \\ &= (4 \times 10^{-6}) (5000) \\ &= 20 \times 10^{-3} \\ &= 20 \text{ mA} \end{aligned}$$

Step 6 of 7

Calculate the current through the current through the capacitor for $2 \text{ ms} < t < 6 \text{ ms}$.

$$\begin{aligned} i(t) &= (4 \times 10^{-6}) \frac{d}{dt} (20 - 5000t) \\ &= (4 \times 10^{-6}) (0 - 5000) \\ &= -20 \times 10^{-3} \\ &= -20 \text{ mA} \end{aligned}$$

Calculate the current through the current through the capacitor for $6 \text{ ms} < t < 8 \text{ ms}$.

$$\begin{aligned} i(t) &= (4 \times 10^{-6}) \frac{d}{dt} (-40 + 5000t) \\ &= (4 \times 10^{-6}) (0 + 5000) \\ &= 20 \times 10^{-3} \\ &= 20 \text{ mA} \end{aligned}$$

Step 7 of 7

Draw the current through the capacitor waveform:

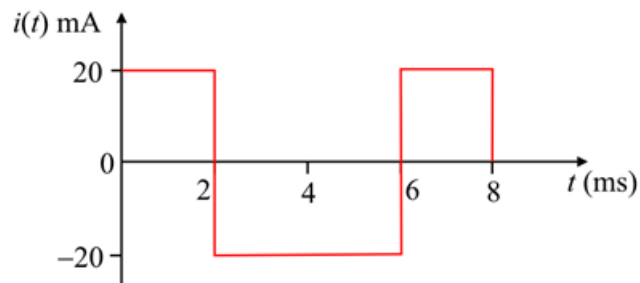


Figure 1