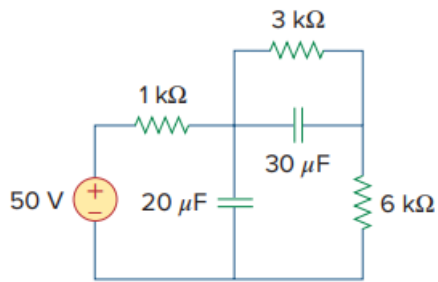


Problem

Under dc conditions, find the energy stored in the capacitors in Fig. 6.13.

Fig. 6.13:



Step-by-step solution

Step 1 of 4

Consider the following RC circuit:

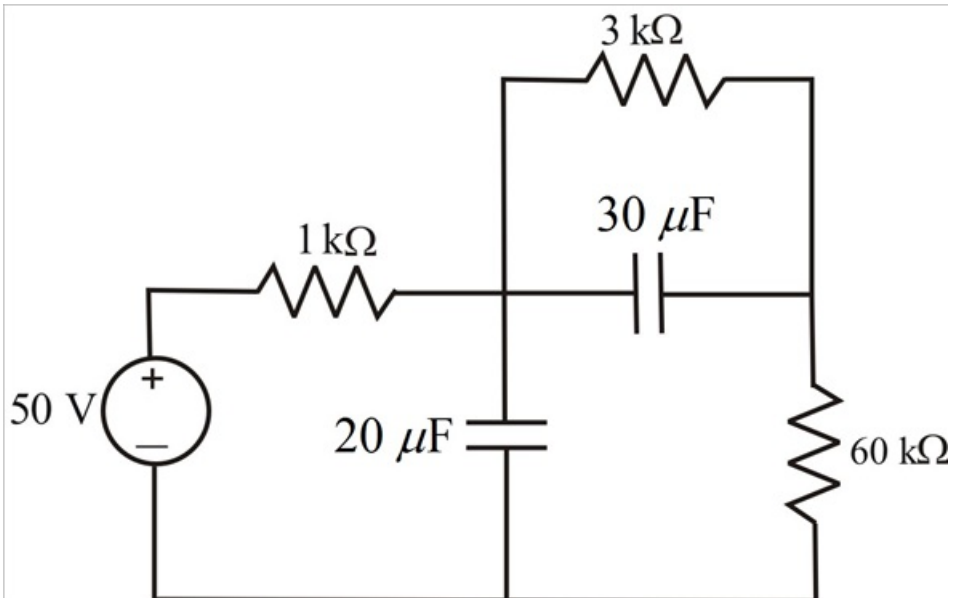


Figure 1

Step 2 of 4

Under the dc conditions, capacitor acts as an open circuit. Redraw the circuit in Figure 1 by replacing the two capacitors with an open circuit.

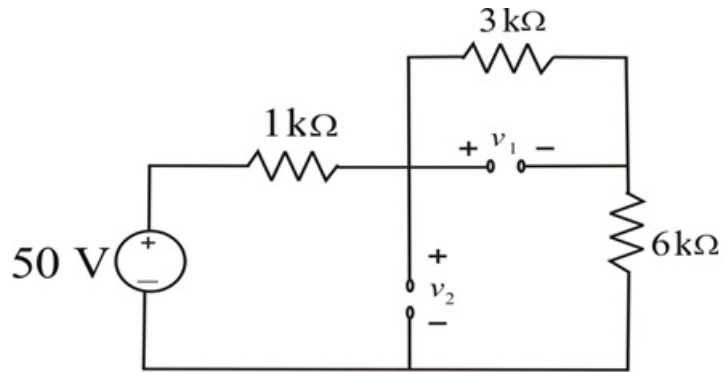


Figure 2

Apply Kirchhoff's voltage law to the closed loop of the circuit in Figure 2.

$$-50 + i \times 1 \times 10^3 + i \times 3 \times 10^3 + i \times 6 \times 10^3 = 0$$

$$i \times 10 \times 10^3 = 50$$

$$i = \frac{50}{10 \times 10^3}$$

$$i = 5 \text{ mA}$$

Determine the voltage v_1 across $3 \text{ k}\Omega$ resistor by using Ohm's law.

$$\begin{aligned} v_1 &= Ri \\ &= (3 \times 10^3)(5 \times 10^{-3}) \\ &= 15 \text{ V} \end{aligned}$$

Determine the voltage v_2 by applying Kirchhoff's voltage law to the loop.

$$-50 + (1 \times 10^3)(5 \times 10^{-3}) + v_2 = 0$$

$$-50 + 5 + v_2 = 0$$

$$v_2 = 45 \text{ V}$$

Step 3 of 4

Determine the energy stored in the capacitor C_1 .

$$\begin{aligned} w_1 &= \frac{1}{2} C_1 v_1^2 \\ &= \left(\frac{1}{2} \right) (30 \times 10^{-6}) (15^2) \\ &= 3.375 \times 10^{-3} \text{ J} \\ &= 3.375 \text{ mJ} \end{aligned}$$

Thus, the energy stored in the capacitor C_1 is **3.375 mJ**.

Step 4 of 4

Determine the energy stored in the capacitor C_2

$$\begin{aligned} w_2 &= \frac{1}{2} C_2 v_2^2 \\ &= \left(\frac{1}{2} \right) (20 \times 10^{-6}) (45^2) \\ &= 20.25 \times 10^{-3} \text{ J} \\ &= 20.25 \text{ mJ} \end{aligned}$$

Thus, the energy stored in the above capacitor C_2 is **20.25 mJ**.