

Chapter 6, Problem 5RQ

Problem

The total capacitance of two 40-mF series-connected capacitors in parallel with a 4-mF capacitor is:

- (a) 3.8 mF
- (b) 5 mF
- (c) 24 mF
- (d) 44 mF
- (e) 84 mF

Step-by-step solution

Step 1 of 1

Answer: (c)

24mF