

Chapter 6, Problem 8RQ

Problem

If the current through a 10-mH inductor increases from zero to 2 A, how much energy is stored in the inductor?

- (a) 40 mJ
- (b) 20 mJ
- (c) 10 mJ
- (d) 5 mJ

Step-by-step solution

Step 1 of 1

6.8

(b)