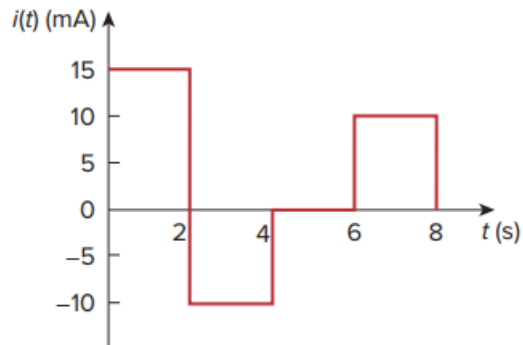


## Problem

A 4-mF capacitor has the current waveform shown in Fig. 6.48. Assuming that  $v(0) = 10$  V, sketch the voltage waveform  $v(t)$ .

**Fig. 6.48:**



## Step-by-step solution

## Step 1 of 4

Refer to figure 6.48 for the waveform given in the textbook.

The initial voltage of the capacitor is,

$$v(0) = 10 \text{ V}$$

From the waveform, the current values are,

$$i(t) = \begin{cases} 15 & 0 < t < 2 \text{ s} \\ -10 & 2 \text{ s} < t < 4 \text{ s} \\ 0 & 4 \text{ s} < t < 6 \text{ s} \\ 10 & 6 \text{ s} < t < 8 \text{ s} \end{cases}$$

The expression for the voltage across the capacitor is,

$$v(t) = \frac{1}{C} \int i dt + v(0) \dots\dots (1)$$

Calculate the voltage across the capacitor for  $0 < t < 2 \text{ s}$ .

Substitute  $4 \times 10^{-3}$  for C, 10 for  $v(0)$ , and  $15 \times 10^{-3}$  for  $i$  in equation (1).

$$\begin{aligned} v(t) &= \frac{1}{4 \times 10^{-3}} \int_0^t (15 \times 10^{-3}) dt + 10 \\ &= \frac{15 \times 10^{-3}}{4 \times 10^{-3}} \int_0^t 1 \times dt + 10 \\ &= 3.75 \times (t) \Big|_0^t + 10 \\ &= (3.75t + 10) \text{ V} \end{aligned}$$

Calculate the voltage at  $t = 2 \text{ s}$ .

Substitute 2 for t.

$$\begin{aligned} v(2) &= 3.75(2) + 10 \\ &= 7.5 + 10 \\ &= 17.5 \text{ V} \end{aligned}$$

## Step 2 of 4

Calculate the voltage across the capacitor for  $2 < t < 4 \text{ s}$ .

Recall equation (1).

$$v(t) = \frac{1}{C} \int i dt + v(0)$$

Substitute  $4 \times 10^{-3}$  for C, 10 for  $v(0)$ , and  $15 \times 10^{-3}$  for  $i$ .

$$\begin{aligned} v(t) &= \frac{1}{4 \times 10^{-3}} \int_2^t (-10 \times 10^{-3}) dt + v(2) \\ &= (-2.5)t \Big|_2^t + 17.5 \\ &= (-2.5t + 5) + 17.5 \\ &= -2.5t + 22.5 \text{ V} \end{aligned}$$

Calculate the voltage at  $t = 4 \text{ s}$ .

$$\begin{aligned} v(4) &= -2.5(4) + 22.5 \\ &= -10 + 22.5 \\ &= 12.5 \text{ V} \end{aligned}$$

### Step 3 of 4

Calculate the voltage across the capacitor for  $4 < t < 6 \text{ s}$ . Recall equation (1).

$$v(t) = \frac{1}{C} \int i dt + v(0)$$

Substitute  $4 \times 10^{-3}$  for C, 10 for  $v(0)$ , and  $15 \times 10^{-3}$  for  $i$ .

$$\begin{aligned} v(t) &= \frac{1}{4 \times 10^{-3}} \int_4^t (0) dt + v(4) \\ &= 0 + 12.5 \\ &= 12.5 \text{ V} \end{aligned}$$

Calculate the voltage across the capacitor for  $6 < t < 8 \text{ s}$ .

$$\begin{aligned} v(t) &= \frac{1}{4 \times 10^{-3}} \int_6^t (10 \times 10^{-3}) dt + v(6) \\ &= (2.5)t \Big|_6^t + 12.5 \\ &= (2.5t - 15) + 12.5 \\ &= (2.5t - 2.5) \text{ V} \end{aligned}$$

Therefore, the voltage across the capacitor is,

$$v(t) = \begin{cases} 10 + 3.75t \text{ V}, & 0 < t < 2 \text{ s} \\ 22.5 - 2.5t \text{ V}, & 2 < t < 4 \text{ s} \\ 12.5 \text{ V}, & 4 < t < 6 \text{ s} \\ 2.5t - 2.5 \text{ V}, & 6 < t < 8 \text{ s} \end{cases}$$

### Step 4 of 4

Draw the waveform of the voltage across the capacitor as shown in figure 1.

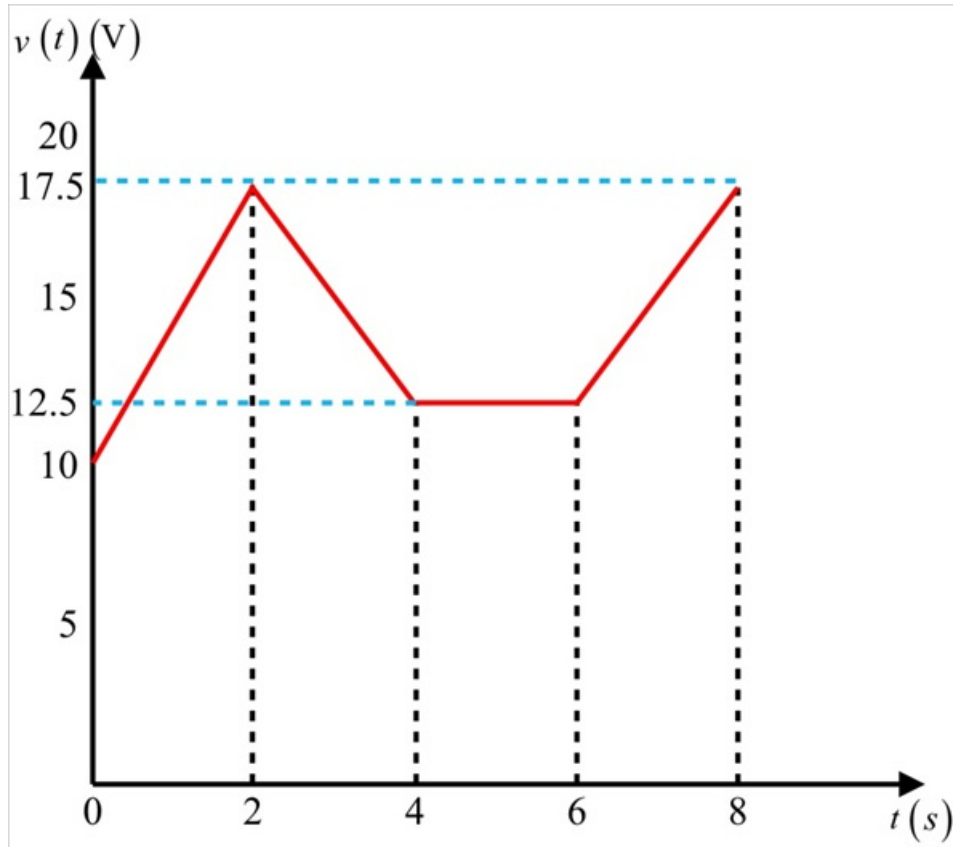


Figure 1