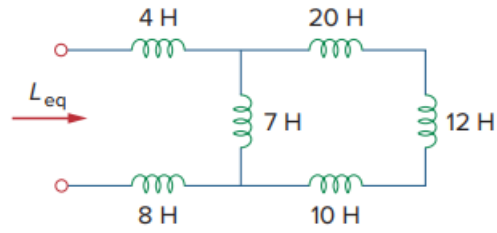


Problem

Find the equivalent inductance of the circuit shown in Fig. 6.31.


Fig. 6.31:



Step-by-step solution

Step 1 of 3

Given circuit

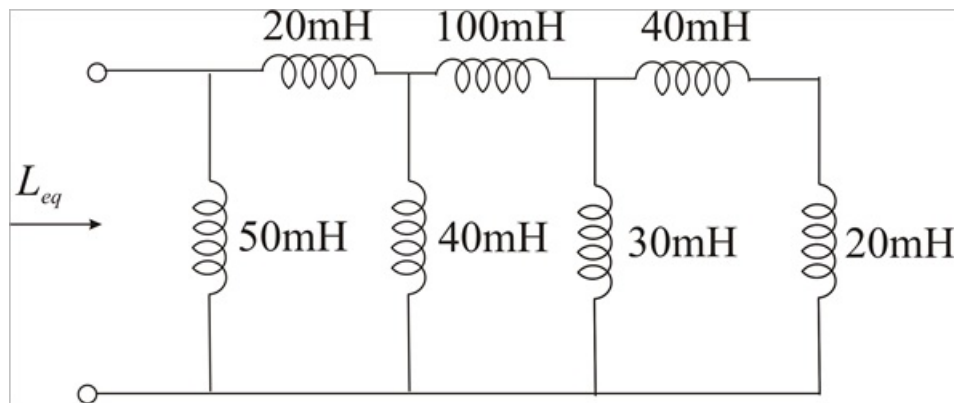

Step 2 of 3

In the above circuit 20mH and 40mH are in series

$$(20 \times 10^{-3}) + (40 \times 10^{-3}) = 60 \text{ mH}$$

This 60mH is in parallel with 30mH

$$60 \text{ mH} \parallel 30 \text{ mH} = \frac{(60 \times 10^{-3}) \times (30 \times 10^{-3})}{(60 \times 10^{-3}) + (30 \times 10^{-3})}$$

$$60 \text{ mH} \parallel 30 \text{ mH} = 20 \text{ mH}$$

Step 3 of 3

This 20mH inductor is in series with 100mH inductor,

$$(20 \times 10^{-3}) + (100 \times 10^{-3}) = 120 \text{ mH}$$

This 120mH inductor is parallel with 40mH inductor.

$$120 \text{ mH} \parallel 40 \text{ mH} = \frac{(120 \times 10^{-3}) \times (40 \times 10^{-3})}{(120 \times 10^{-3}) + (40 \times 10^{-3})}$$

$$120 \text{ mH} \parallel 40 \text{ mH} = 30 \text{ mH}$$

This 30mH inductor is in series with 20mH inductor

$$(30 \times 10^{-3}) + (20 \times 10^{-3}) = 50 \text{ mH}$$

This 50mH inductor is in parallel with the 50mH inductor,

Hence

$$L_{eq} = \frac{(50 \times 10^{-3}) \times (50 \times 10^{-3})}{(50 \times 10^{-3}) + (50 \times 10^{-3})}$$

$$\therefore \boxed{L_{eq} = 25 \text{ mH}}$$