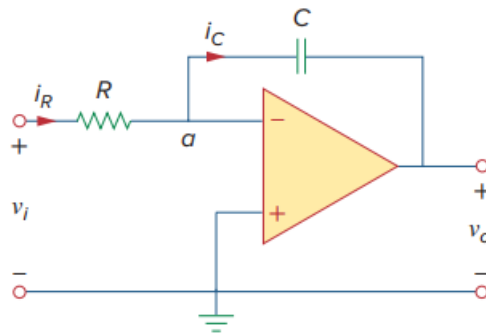


Problem

The integrator in Fig. 6.35(b) has $R = 100 \text{ k}\Omega$, $C = 20 \text{ }\mu\text{F}$. Determine the output voltage when a dc voltage of 2.5 mV is applied at $t = 0$. Assume that the op amp is initially nulled.

Fig. 6.35(b): Replacing the feedback resistor in the inverting amplifier in (a) produces an integrator in (b).



Step-by-step solution

Step 1 of 3

Consider the following integrator circuit:

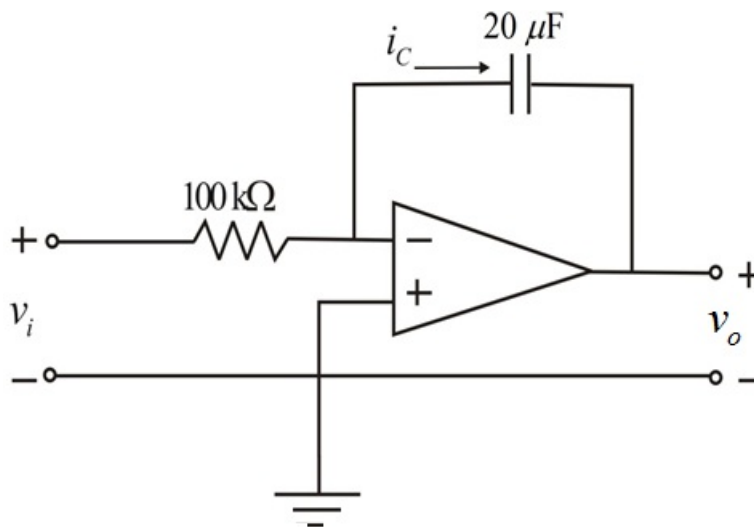


Figure 1

Step 2 of 3

The dc voltage, $v_i = 2.5 \text{ mV}$ at $t = 0$.

The current through the resistor is equal to that in the capacitor, that is, $i_R = i_C$ because both resistor and capacitor are in series.

$$\begin{aligned} i_R &= \frac{v_i}{R} \\ &= \frac{2.5 \times 10^{-3}}{100 \times 10^3} \\ &= 2.5 \times 10^{-8} \text{ A} \end{aligned}$$

Step 3 of 3

Write the formula for capacitor current.

$$i_c = -C \frac{dv_o}{dt}$$

Here $i_R = i_C$.

Thus,

$$\frac{v_i}{R} = -C \frac{dv_o}{dt}$$

$$\begin{aligned} dv_o &= \left(-\frac{1}{RC} \right) v_i dt \\ &= \left(-\frac{1}{100 \times 10^3 \times 20 \times 10^{-6}} \right) (2.5 \times 10^{-3}) dt \\ &= -0.5 \times 2.5 \times 10^{-3} dt \\ &= -1.25 \times 10^{-3} dt \end{aligned}$$

Integrate the equation to get the output voltage.

$$\begin{aligned} v_o &= -1.25 \times 10^{-3} t \text{ V} \quad \text{Thus, the output voltage, } v_o \text{ of the integrator circuit is } \boxed{-1.25t \text{ mV}}. \\ &= -1.25t \text{ mV} \end{aligned}$$