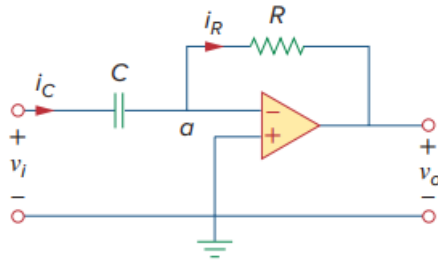


Problem

The differentiator in Fig. 6.37 has $R = 100 \text{ k}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$. Given that $v_i = 5t \text{ V}$, determine the output v_o .

Fig. 6.37: An op amp differentiator.



Step-by-step solution

Step 1 of 2

Consider the following differentiator circuit:

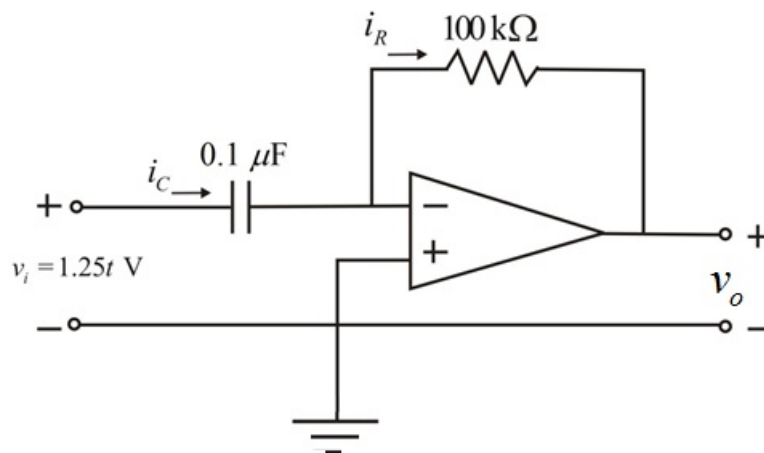


Figure (1)

Step 2 of 2

The dc voltage, $v_i = 1.25t \text{ V}$

Write the formula for output voltage, v_o .

$$v_o = -RC \frac{dv_i}{dt}$$

The current through the resistor is equal to that in the capacitor, that is, $i_R = i_C$ because both resistor and capacitor are in series.

Thus,

$$\begin{aligned} v_o &= -(100 \times 10^3)(0.1 \times 10^{-6}) \frac{d}{dt}(1.25t) \\ &= (-0.01)(1.25) \\ &= -0.0125 \\ &= -12.5 \text{ mV} \end{aligned}$$

Thus, the output voltage, v_o is -12.5 mV.