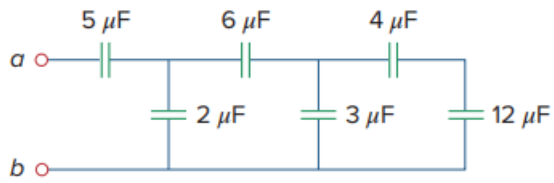


Problem

Determine the equivalent capacitance at terminals a - b of the circuit in Fig. 6.55.

Fig. 6.55:



Step-by-step solution

Step 1 of 1

$$4\ \mu\text{F} \text{ in series with } 12\ \mu\text{F} = (4 \times 12) / 16 = 3\ \mu\text{F}$$

$$3\ \mu\text{F} \text{ in parallel with } 3\ \mu\text{F} = 6\ \mu\text{F}$$

$$6\ \mu\text{F} \text{ in series with } 6\ \mu\text{F} = 3\ \mu\text{F}$$

$$3\ \mu\text{F} \text{ in parallel with } 2\ \mu\text{F} = 5\ \mu\text{F}$$

$$5\ \mu\text{F} \text{ in series with } 5\ \mu\text{F} = 2.5\ \mu\text{F}.$$

$$\text{Hence } C_{eq} = 2.5\ \mu\text{F}$$